

29.11 ELECTRICITY (448)

29.11.1 Electricity Paper 1 (448/1)



MANYAM FRANCHISE
Discover! Learn! Apply

SECTION A (52 marks)

Answer all the questions in this section.

- 1 (a) State three conditions required for combustion to take place.
(b) Name three types of fire extinguishers. (3 marks)
- 2 (a) List four types of institutions which offer craft certificate courses in electrical engineering. (2 marks)
(b) Explain the cause of a dry joint on a printed circuit board. (2 marks)
- 3 (a) Name four types of capacitors. (2 marks)
(b) Two capacitors having capacitance of $6 \mu\text{F}$ and $4 \mu\text{F}$ are connected in series across a 200V dc supply.
Calculate the:
(i) voltage across each capacitor;
(ii) charge on each capacitor. (4 marks)
- 4 (a) Name two types of secondary cells. (1 mark)
(b) Six cells each of emf 1.5V and internal resistance of 1.2Ω are connected in parallel to supply a load of 10Ω . Calculate the current through the load. (3 marks)
- 5 (a) Determine the resistance of carbon resistor whose colour codes are:
(i) green, yellow, brown, gold;
(ii) blue, orange, red. (4 marks)
(b) The current through a 0.5H coil of inductance changes 6A to 3A in 0.04 seconds. Calculate the value of e.m.f induced in the coil. (2 marks)
- 6 (a) State three characteristics of lines of magnetic flux. (3 marks)
(b) State the function of each of the following features of analogue instruments:
(i) deflecting;
(ii) controlling;
(iii) damping. (3 marks)
- 7 (a) Give three reasons why copper is commonly used as a conductor material in electrical installations. (3 marks)
(b) State two advantages of light gauge pvc conduits over the heavy gauge pvc conduits. (2 marks)

- 8 (a) Compare **two** operational characteristics of silicon diode and Germanium diodes. (2 marks)
- (b) Sketch a half wave rectifier and its output waveform. (3 marks)
- 9 (a) Sketch a diagram of four pole dc machine and label five main parts. (5 marks)
- (b) State **one** possible cause of each of the following symptoms:
- (i) motor will not reach full speed;
 - (ii) iron box overheats;
 - (iii) fluorescent lamp flickers continuously. (3 marks)

10 Figure 1 shows an oblique view of a stepped block.

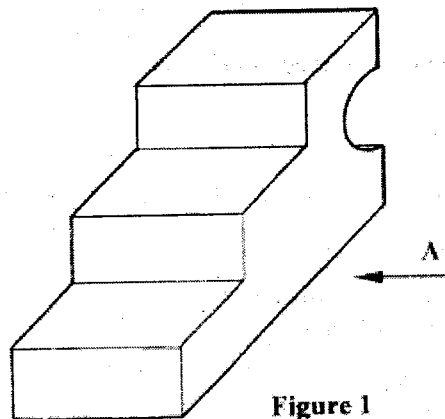


Figure 1

Sketch in first angle projection the three orthographic views taking the front elevation in the direction of arrow A. (5 marks)

SECTION B (48 marks)

Answer any **four** questions from this section.

- 11 (a) With the aid of a labelled diagram, explain the operation of a single phase transformer. (8 marks)
- (b) A 200 KVA, 11000v/240v 5Hz single phase transformer has 600 turns on the primary side. Calculate:
- (i) the primary and secondary currents;
 - (ii) the number of secondary turns. (4 marks)

- 12 (a) Show that the total resistance of two resistors connected in parallel is equal to the product of their resistance divided by the sum of their resistance. (2 marks)
- (b) State the meaning of the following terms as applied to alternating current:
 (i) frequency;
 (ii) amplitude;
 (iii) periodic time. (3 marks)
- (c) A coil of inductance 30mH and 5Ω resistance is connected across a 240 volt 50 Hz supply. Calculate the:
 (i) circuit current;
 (ii) phase angle;
 (iii) power factor;
 (iv) apparent power;
 (v) active power. (7 marks)
- 13 (a) List three metal parts that are exempted from earthing in a domestic installation. (3 marks)
- (b) Give three reasons why a verification of polarity test is carried out in a completed domestic installation. (3 marks)
- (c) Draw a line diagram of a national grid system showing typical voltages at each stage. (6 marks)
- 14 With the aid of a diagram, describe the construction and operation of a moving coil instrument. (12 marks)
- 15 (a) Draw a labelled circuit diagram of a PNP transistor amplifier in common base configurations. (3 marks)
- (b) Table 1 below shows a bill of materials used to construct a stabilized dc supply.

No	Description of material	Quantity
1	Double pole switch	1
2	Double wound transformer	1
3	Rectifier diodes	4
4	Electrolytic capacitor	1
5	Carbon resistors	1
6	Zener diode	1
7	Connecting wires	Several

Draw a circuit diagram of the power supply. (9 marks)

29.11.2 Electricity Paper 2 (449/2)

EXERCISE 1

Using the components, materials and equipment provided, connect the circuit as shown in figure 1. (4 marks)

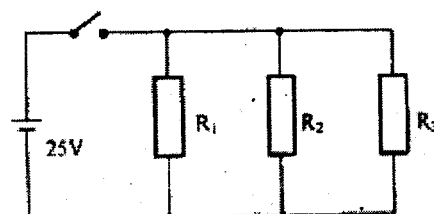


Figure 1

- (a) Measure and record the total circuit current I_T (1 ½ marks)

I_T

- (b) Measure and record the current through each of the following resistors.

R_1 (mA)

R_2 (mA)

R_3 (mA) (4 ½ marks)

- (c) In the circuit:

(i) replace R_3 with R_4 (2 marks)

(ii) repeat step (a) above (1 ½ marks)

I_T

- (iii) repeat step (b) above and record the following:

R_1 (mA)

R_2 (mA)

R_3 (mA) (4 ½ marks)

- (d) (i) State the effect on the current when R_3 is replaced with R_4 .

(1 mark)


- (ii) State the relationship between total circuit current (I_T) and the branch current.

(1 mark)


EXERCISE 2

Use the tools, equipment and materials provided to make the object shown in figure 2.


(20 marks)

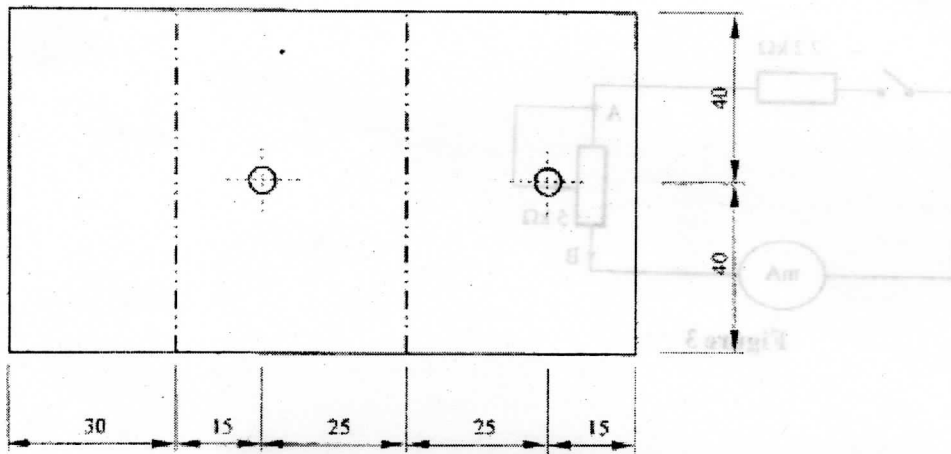

PART A

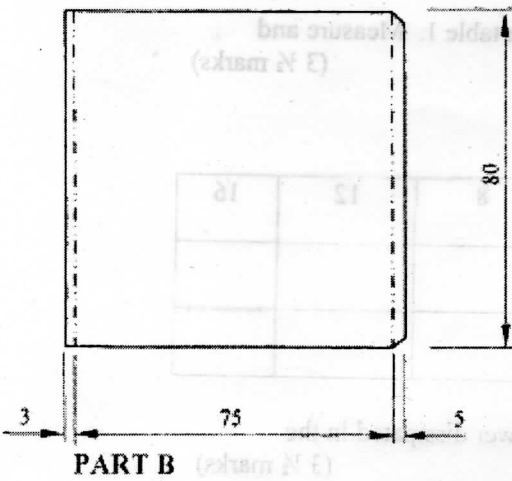

PART B

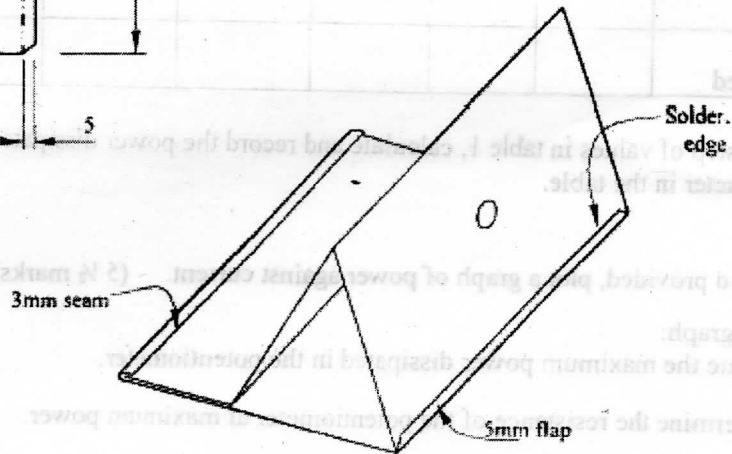

EXERCISE 3

Using the components, materials and equipment provided, connect the circuit as shown in figure 3.

(5 ½ marks)

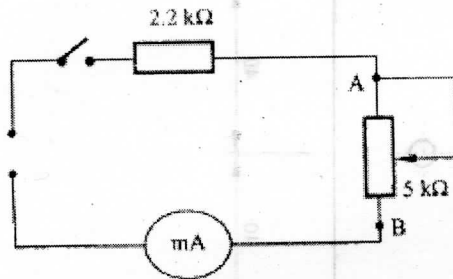


Figure 3

Perform the following tasks:

- (a) Vary the potentiometer to obtain each of the voltages shown in table 1. Measure and record corresponding currents. (3 ½ marks)

Table 1

Voltage (v) across AB	0	2	4	6	8	12	16
Current (mA)							
Power Dissipated							

- (b) For each step of values in table 1, calculate and record the power dissipated in the potentiometer in the table. (3 ½ marks)
- (c) On the grid provided, plot a graph of power against current. (5 ½ marks)
- (d) From the graph:
- state the maximum power dissipated in the potentiometer.
 - determine the resistance of the potentiometer at maximum power.

(2 marks)

EXERCISE 4

Figure 4 shows a block diagram of the prefabricated transistor amplifier circuit provided.

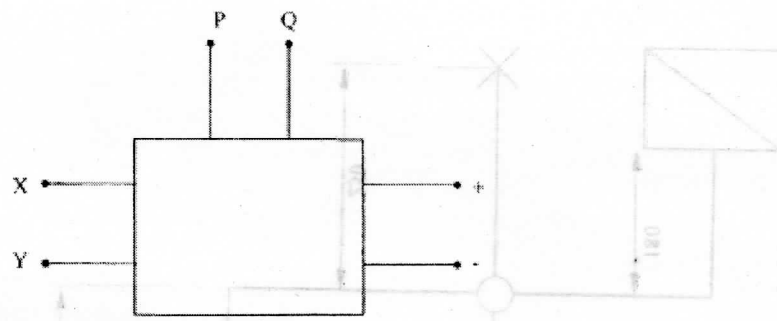


Figure 4

Perform the following tasks:

- (a) Connect:
 - (i) the microammeter to points PQ to measure base current.
base current:.....
 - (ii) the milliammeter to points XY to measure collector current.
collector current: (2 marks)
- (b) Turn the switch to the ON position.
- (c) Adjust R_L to obtain each of the base current values in table 2. Measure and record the corresponding collector current.

Table 2

BASE CURRENT (μA)	COLLECTOR CURRENT (μA)
10	
20	
30	
40	
50	

(5 marks)

- (d) Using the values in table 2, plot the graph of I_C against I_B . (4½ marks)
- (e) From the graph, determine the Beta (β) of the transistor. (2 marks)
- (f) Draw a schematic diagram of the circuit. (6½ marks)

EXERCISE 5

Figure 5 shows a layout of a lighting circuit. Using PVC sheathed wiring system, install the circuit such that the lamp is controlled independently by S_1 and S_2 . (20 marks)

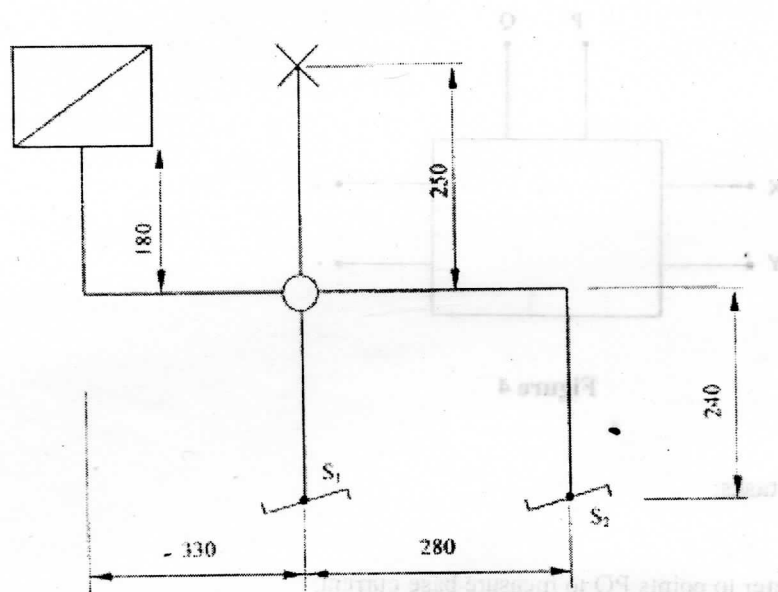


Figure 5

BASE CURRENT (mA)	COLLECTOR CURRENT (mA)
10	
20	
30	
40	
50	