

30.19 ELECTRICITY (448)

30.19.1 Electricity Paper 1 (448/1)

- 1 (a)
- Never switch on an electric source if a person is leaning on the equipment.
 - Don't use such tool in damp areas.
 - Ensure the tool is earthed.
 - Remove plug from the socket when equipment is not in use.
 - Ensure all electrical connections are safe. *(Any 3x½ = 1 ½ marks)*
- (b)
- Avoid storage in excessive heat.
 - Avoid dampness.
 - Remove dry cells.
 - Screen from magnetism.
 - Avoid dusty environment. *(Any 3x½=1 ½ marks)*
- (c) Artisan, Craftsman, Technician, Engineer. *(4x ½ =2 marks)*
2. (a) File will remove tin coating thus causing copper to dissolve in hot solder. *(1 mark)*
- (b) (i) **Short circuit**:- load cannot draw current because it is bypassed by a conductor.
(ii) **Overload**:- the current through the load is too large because resistance is too low for the rated load. *(2x1 marks)*
- (c) (i) **Resistance**:- impedes or reduces current in a circuit.
(ii) **Inductance**:- opposes change of current. *(2x1 marks)*
3. (a)
- Are lighter than copper cables.
 - Are cheaper than copper cables.
 - Are more corrosion resistance than copper. *(Any 2x1=2 marks)*
- (b) Current for solar panel is $I = \frac{40\text{w}}{12\text{v}}$
 \therefore rate of charge = $\frac{40}{12} \times 6 \text{ AH/day}$
No. of days required for full charge is
 $\frac{60 \text{ A-h}}{\frac{40}{2} \times 6} = \frac{60}{20} = 3 \text{ days}$ *(4 marks)*
4. (a) Potential energy → Kinetic energy → Mechanical energy → Electrical energy *(4x½ =2 marks)*
- (b) Length of the wire is given.

$$l = \frac{aR}{P}$$

$$a = \pi \left(\frac{D}{2} \right)^2 = \frac{\pi D^2}{4}$$

$$\therefore l = \frac{\pi D^2 R}{4P}$$

$$= \frac{3.14 \times (1.0 \times 10^{-3} \times 150\text{m})}{4 \times 75 \times 10^{-6}}$$

$$= 1.57\text{m}$$


(5 marks)

5. (a) Iron, Nickel, Cobalt, Aluminium, Copper. (Any 2 $\times \frac{1}{2}$ = 1 mark)
- (b) Done by placing the magnet inside a solenoid through which current is flowing. With the current still flowing, the magnet is slowly withdrawn from the solenoid. (2 \times 1 = 2 marks)
6. (a) Electric power is transmitted at high voltage in order to reduce current and therefore reduce cable sizes, power loss and cost. (2 marks)
- (b)
- **Isolation**:- switching off all conductors connecting to the supply.
 - **Circuit protection**:- automatically disconnects installation when current exceeds normal.
 - Protection against leakage of current to earth. (3 \times 1 = 3 marks)
7. (a)
- **Communicator segments**:- copper.
 - **Slip ring**:- brass.
 - **Brushes**:- carbon or copper.
 - **Armature core**:- iron lamination. (4 $\times \frac{1}{2}$ = 2 marks)
- (b)
- Due to low resistance excess current would flow damaging the motor.
 - There would be very low current in field coils causing the armature to race. This can lead to damage due to centrifugal forces.
 - There would be no back e.m.f. causing excess current to flow and possibly damaging the motor. (3 \times 1 = 3 marks)
8. (a) Find the terminal which shows continuity with the tab.
- (b) With ohmmeter lead on collector, touch the negative lead on each of the other terminals. Terminal showing low resistance in the base.
- (c) The emitter is the terminal showing open circuit condition with the collector. (3 \times 1 = 3 marks)
9. (a)
- Increasing the number of its coil.
 - Using stronger magnet.
 - Using weaker hairspring or a wire suspension.
 - Using a long beam of light as a pointer. (3 \times 1 = 3 marks)
- (b) (i)
- Loose control knob.

- Faulty thermostat element.
- Incorrect wiring. (2x ½ =1 marks)

- (ii)
- Check the temperature control knob for tightness.
 - Open the iron box and check the thermostat.
 - Check the wiring for correctness.
 - Logical sequence. (4x ½=2 marks)

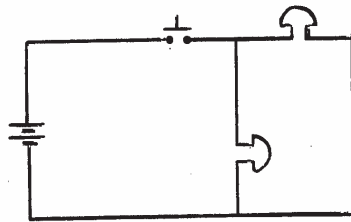10. (a) **Detail drawing** shows the parts with their sizes, materials, shapes etc.
- (b) **Exploded drawing** shows the sequence in which all the parts are put together in the final assembly. (2x1=2 marks)



(5 marks)

11. (a)
- Assuming the motor has been operating at moderate speed, when it is suddenly subjected to a heavier load, the first effect is to slow down the motor.
 - Slowing the motor reduces back emf generated because back emf is directly proportional to speed.
 - Reduced back emf makes the line voltage to push more current through the motors' field coils.
 - More current in the field coils produces a stronger magnetic field.
 - Because torque depends on the product of both magnetic field and flux, both will therefore increase and so will the torque. (5x1=5 marks)

(b) (i) Transformation ration = $\frac{E_p}{E_g} = \frac{240v}{120v} = 2$ (1 mark)

(ii) $I_s = \frac{KVA}{E_s} = \frac{1200}{120} = 10A$ (1 mark)


(iii) Primary impedance (Z_p) = $a^2 Z_l$ (1 mark)

Secondary impedance (Z_l) = $\frac{120v}{10A} = 12\Omega$ (1 mark)

$a = z \therefore Z_p = Z^2 \times 12 = 48\Omega$ (1 mark)

(iv) No. of secondary coil turns
 $= \frac{E_s}{\text{Rate per turn}} = \frac{120}{0.2 \text{ per turn}} = 600 \text{ turns}$ (2 marks)

- 12 (a) V-1 curve of rectifier diode

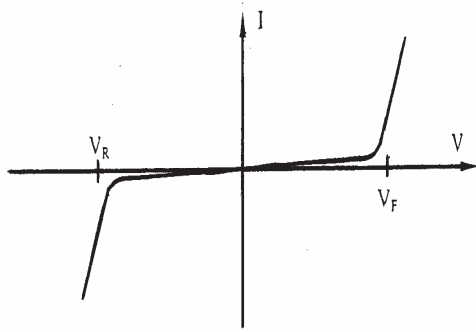

(4 marks)

- (b) (i) Value of resistor

$$R_s = V = V_{in} - V_Z = (12 - 6.5)$$

$$I = I_Z + I_L = (100 + 10) \text{mA}$$

(1 mark)

$$R_s = \frac{5.5}{110 \text{mA}} = \frac{5.5 \text{V}}{0.11 \text{A}} = 50 \Omega$$

(1 mark)

$$\text{Power dissipated RL} = V_Z I_L$$

$$= 6.5 \times 0.1 \text{A} = 0.65 \text{W}$$

(2 marks)

(ii)


- Since V_Z remains constant V_R decreases
- I_L remains constant
- I_Z decreases

(3x1=3 marks)

13. (a) **Stroboscopic effect:** is a phenomenon whereby reversing discharge of ions and electronics by the lamp coincides with the speed of a revolving machine such that the machine appears to be stationary.

(2x1=2 marks)

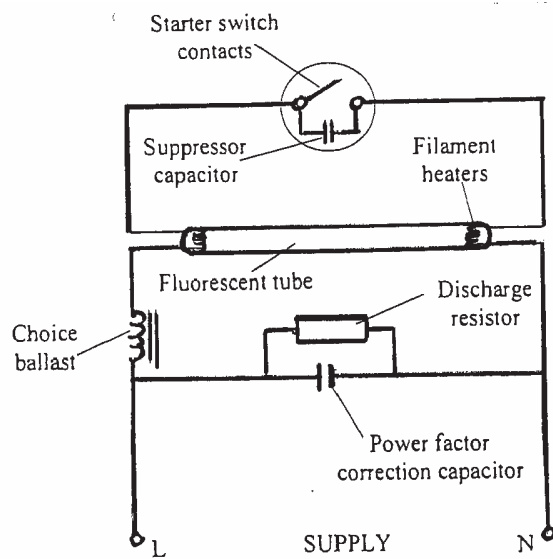- (b) (i) Starter switch operated fluorescent lamp



(7 marks)

- (ii) **Choke:** induces a high voltage which enables a discharge to be initiated between the electrodes of the tube when the starter contacts open. It also keeps the discharge and lamp current at a steady value when lamp is in operation.

Flourescent Powder: converts the ultra violet light emitted by the discharge and melting mercury to drop to a shadowless white or coloured light.

(2 x 1 ½ marks)

14. (a) (i) When S is open

$$\text{I} \quad \text{Voltage } V_A = \frac{(R_1 + R_2)}{(R_3 + R_1 + R_2)} V_S \quad (1 \text{ mark})$$

$$= \frac{4\text{k}\Omega}{6\text{k}\Omega} \times 18\text{v} \quad (1 \text{ mark})$$

$$= 12\text{V} \quad (1 \text{ mark})$$

$$\text{II} \quad \text{Current } I_6 = \frac{V_s}{R_5 + R_6} \quad (1 \text{ mark})$$

$$= \frac{18\text{v}}{3\text{k}\Omega} = 6\text{mA} \quad (1 \text{ mark})$$

- (ii) No current flows because a balanced wheatstone bridge is formed (1 mark)

- (b) (i) Equivalent capacitance, C_T

$$C_T = \frac{C_1 \times C_2}{C_1 + C_2} \quad (1 \text{ mark})$$

$$= \frac{9 \times 6}{9 + 6} = \frac{54}{15} \quad (1 \text{ mark})$$


$$= 3.6\mu\text{F} \quad (1 \text{ mark})$$

- (ii) Current in the circuit, i

$$\begin{aligned}
 i &= \frac{es}{Z} && (1 \text{ mark}) \\
 &= \frac{es}{\sqrt{R^2 + X_c^2}} && (1 \text{ mark}) \\
 &= \frac{10}{\sqrt{3^2 + 6^2}} && (1 \text{ mark}) \\
 &= i=11.5\text{mA} && (1 \text{ mark})
 \end{aligned}$$

15. (a)
- Draw for schematic diagram of the circuit.
 - Draw the PCB artwork.
 - Transfer artwork to copper side of the board.
 - Etch the board.
 - Drill holes for the component.
 - Position the components and connectors.
 - Solder the components and connectors.
 - Dress the PCB that is, cut out the tails and close PCB surface.
- (8x ½ =4 marks)

(b)

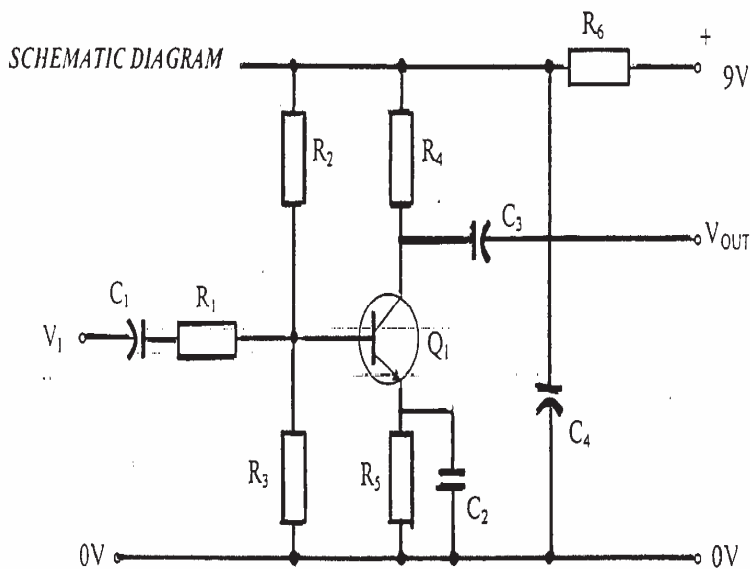

(8 marks)

30.20 DRAWING AND DESIGN (449)

30.20.1 Drawing and Design Paper 1 (449/1)

1. (a) **Grid paper** : used in the initial setting of a drawing by tracing. It saves time.
Tracing paper: used for copying or developing existing drawings. It saves time. (2 × 1 = 2 marks)
- (b) **Engineer**
- Designs structures and components.