

30.20 ELECTRICITY (448)
30.20.1 Electricity Paper 1 (448/1)



1. (a) **PROCEDURE**
 Switch off the supply or use a non-conductor to remove the victim from live conductor.
 Place the victim in a comfortable position.
 Call for medical assistance.
 Apply first aid if necessary. 4 x ½ = 2 marks
Sequence = 1
- (b) **ELECTRICAL TECHNICIAN**
 Supervises those below him
 Trains those below him
 Manages workshop production line
 Assist workers when they encounter challenges
Any 4 x ½ .
2. (a) **DRILLING A HOLE**
 Measure and mark the position of the hole.
 Centre punch the hole.
 Mount the work firmly in a vice.
 Using the correct size of drill to drill the hole. 4 x ½
- (b) **PARTS OF A BATTERY**
 Positive plates consist of lattice type of grid of cast antimony lead alloy covered with lead peroxide.
 Separators are thin sheets of porous insulators placed between positive and negative plates.
 Casing made of vulcanized rubber, ebonite, plastic etc molded into partitioned container.
3 x 1
3. (a) **METHOD OF GENERATING ELECTRICITY**
 Hydro
 Geothermal
 Diesel engines
 Thermal 4 x 2
- (b) Self inductance comprises one coil changing current which induces emf in itself while in mutual induction, 2 coils which are close changes current in one induced emf into the other.
(1½ x 2)
- (c) Total charge $CT = \frac{C_1 C_2}{C_1 + C_2} = \frac{8 \times 12}{12 + 8} = 4.8 \mu F$ (1½ marks)Ω
 $Q = C_T \times V = 50 \times 4.8 \times 10^{-6} = 240 \mu C$ (1½ marks)
4. (a) **RC Time Constant**
 Is the time taken to charge the capacitor to 63.2% of the charging voltage. (1 mark)
- (b) (i) $RT = 4 + 2 + \frac{12 \times 6}{12 + 6} = 6 + 4 = 10 \Omega$ (2)
 $TT = \frac{V}{R} = \frac{10}{10} = 1 \text{ Amp}$ (1)
 $P = I^2 R = 1^2 \times 20 = 2 \text{ w}$ (1)
5. (a) **Ac Machines Types**
 Revolving armature
 Revolving field 2 x ½
- (b) **Parts of Induction motor**
 Startor
 Winding
 Squirrel cage rator
 Bearing

- (c) Frame/Yoke/Bod Any 4 x ½
 No. of pairs = $\frac{60F}{\text{rpm}} = \frac{60 \times 50}{1500} = 2$ pairs .

6. (a) $R_T = \frac{V}{I_{f.s.d}} = \frac{1.5}{50 \times 10^{-6}} = 0.03 \times 10^6 = 31 \Omega$


- (b) Advantage of digital measuring instrument
 High sensitivity
 Easy to read
 More rugged and robust (withstands rough handling)
 No effect from stray magnetism

Any 3 x ½

- (c) Identifying Faults
 Physical inspection by looking at the circuit components to determine any change in colour, shape, e.t.c.

Circuit analysis – by taking measurements and comparing with what is in the service manual.
 2 x 1

7. Magnetic flux

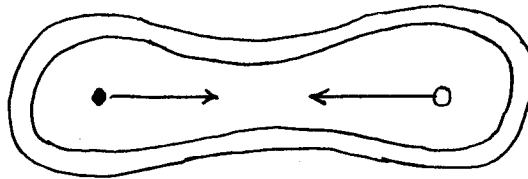

Polarity = 1
 Pattern = 1
 Force direction = 1


8. (a) Final Circuit
 Outgoing circuit in a consumer unit (CU) to supply electrical directly via socket outlet.
 (1 mark)

- (b) Regulations
 (i) The total number of spurs stationery appliances shall not exceed the total number of socket outlets.
 (ii) The rating of fuse or circuit breaker should be 30A.
 (iii) Maximum floor area should be 100m².
 (iv) No standar 13A socket installed inside the bathroom
 (v) Only 2.5mm² cables should supply the 13A socket.

Any 4 x 1


9. (a) Zener voltage
 This is the point at which the zener diode breaks down when connected in reverse bias.
 The voltage remains almost constant as the load current varies 2 x 1

- (b) PNP Transistor

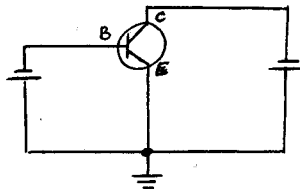



Correct PNP symbol = 1
 "Terminal connections = 1½
 Grounding/earthing = ½

10.

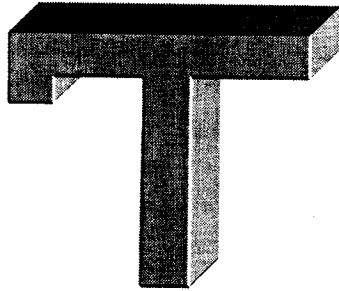

Correct sketch= 2
 Oblique=1
 Proportion = 1
1

11.

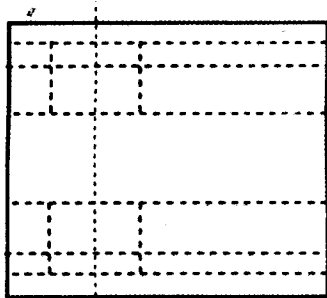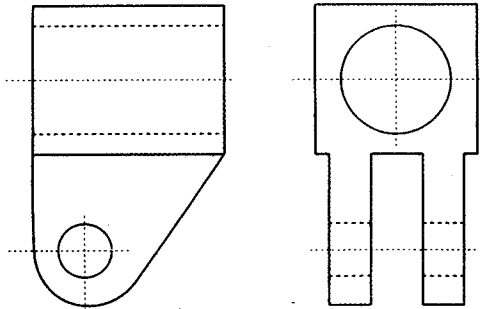

FE
 Faces (3 x 1) = 3
 Hidden details = 1
 EE
 Faces (3 x 1) = 3
 Hidden details = 1
 Centre lines = 2
 First angle projection = 1
 Neatness = 1
12

12.

- (a) Transistor
 Power transistors are larger in size and usually have a heat sinks. 2 x 1
- (b) Transistor ratio
 DC ALPHA is the ratio of the emitter current to the collector current in a dc circuit.
 2 x 1

AC BETA is the ac current gained in a common emitter amplifier. It is the ratio of the change in the output (collector) current to the change in the input (base) current.

2 x 1

$$(c) \quad \beta = \frac{I_C}{I_B} \Rightarrow 100 = \frac{10 \text{ mA}}{I_B} \quad (1)$$

$$\therefore I_B = \frac{10 \text{ mA}}{100} = 0.0001 \text{ mA or } 100 \mu\text{A}$$

From the diagram.

$$V_{CC} = I_B R_B + V_{BE} \quad 20\text{V} = I_B R_B + 0.7\text{V}$$

$$I_B R_B = (20 - 0.7) = 19.3\text{V}$$

$$R_B = \frac{19.3}{I_B} = \frac{19.3}{100 \mu\text{A}} = 193 \text{K}\Omega$$

$$I_C R_C = V_{CC} - V_{CE}$$

$$R_C = \frac{V_{CC} - V_{CE}}{I_C}$$

$$= \frac{(20 - 10)}{0.01 \text{ A}} = \frac{10}{0.01} = 1 \text{K}\Omega$$

13. (a) Fusing Current is the minimum current that will cause the fuse element to melt or blow while

Current Rating is the maximum current the fuse is designed to carry for indefinite period without deterioration of its element.

2 x 1

- (a) Disadvantages

Oxidation of fuse element

Dangers of replacing with incorrect wire


Unreliable – takes time to melt

Higher fire risk due to concentration of heat

Doesn't discriminate high transient current and continuous high current.

Any 2 x 1

- (b) Single Stroke Electric Bell

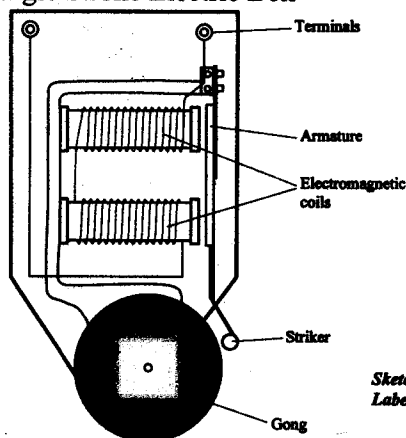

Sketching = 2
Labelling (4x 1/2) = 2

Operation

When the push button is pressed, the circuit is completed and current flows to energize electromagnetic coil. The coil creates a magnetic field around it and attracts the soft iron armature.

The armature moves towards the electromagnets to the gong and remains in that position until the push button is released.

4 x 1


14. (a) Sine Wave
 $f = \frac{1}{T} = \frac{1}{100 \times 10^{-3}} = \frac{10^3}{100} = 10\text{Hz}$ (1½ marks)

(b) Current I_1 , and I_2
 $X_L = 2\pi fL = 2\pi \times 50 \times 0.38 = 119.3\Omega$ (1½ marks)

$I_1 = \frac{V}{R} = \frac{240}{100} = 2.4\text{A}$ (1½ marks)

$I_2 = \frac{V}{X_L} = \frac{240}{119.3} = 2.01\text{A}$ (1½ marks)

Phaser Diagram

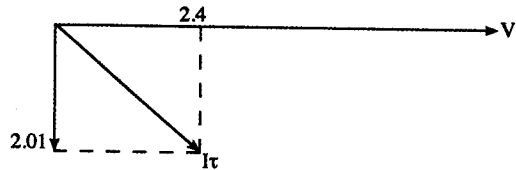


$I_T = \sqrt{2.4^2 + 2.01^2} = \sqrt{5.76 + 4.04} = 3.3\text{A}$ (2 marks)

Power factor $\text{Pf} = \frac{R}{Z} = \frac{100}{133} = 0.766$ (1 mark)

Phase angle $= \cos^{-1} 0.766 = 40^\circ$ (1 mark)

15.

(a)

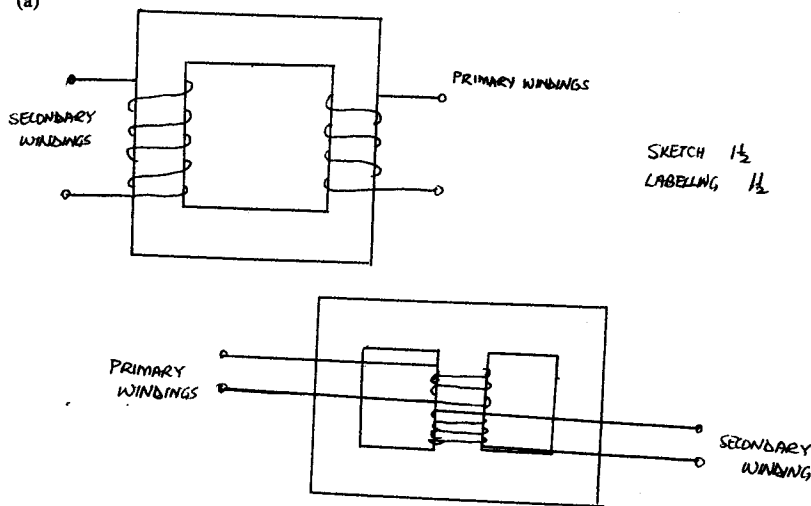

1

(b) (i) $I_s \frac{P}{V_s} = \frac{10}{12}\text{A}$
 $I_s \frac{P}{V_s} = \frac{10}{12}\text{A}$

$I_p = \frac{V_s}{V_p} \times \frac{I_s}{\text{efficient}}$
 $= \frac{12}{40} \times \frac{10}{12} \times \frac{100}{96}$
 $= 0.0434\text{A}$
 $= 43\text{mA}$

1

½

$$\begin{aligned} \text{(ii) Input power} &= V \times I = 240 \times 0.0434 \\ &= 10.42\text{w} \end{aligned}$$

$$\begin{aligned} \text{Power loss} &= \text{input power} - \text{output power} \\ &= 10.42 - 10 \\ &= 0.42\text{w} \end{aligned}$$

1½1

1½1