

25.0 ELECTRICITY

25.1 Electricity Paper 1 (448/I)

1. (a) Safety precautions

Do not climb electric power posts
Avoid touching any broken overhead cable
Do not climb trees near overhead cables
Avoid felling trees near overhead power lines
Never erect building below power lines.

(Any 3 x 1)

(b) Areas of specialisation

Electrical (power option)
Electronics
Telecommunication
Instrumentation

(4 x ½)

2. (a) Tools

Hacksaw
Scriber
Steel rule
Try square
Tape measure
Chisel

Dot punch
(Any 4 x ½)

(b) Magnetic lines of force

Each line forms a closed loop
Lines never intersect
Stretched elastic cords always trying to shorten themselves
Direction of line is that of north-seeking pole

(Any 3 x 1)

3. (a) Inductor cores

Air core
Ferrite core
Iron core

(Any 2 x ½)

(b) Silver

is very expensive/ rare
not mechanically strong

(2 x 1)

4. (a) Resistance

(i) $630 \Omega \pm 10\%$
(ii) $820 \text{ k}\Omega \pm 20\%$
(iii) $59 \Omega \pm 5\%$

(3 x 1)

(b) Inductance of a coil

Number of turns in a coil
Length of the coil
Cross-section area of the coil
Relative permeability of the core

(Any 2 x 1 = 2 marks)

5. (a) **Determining polarity**
 The terminal at the crimped end of capacitor is the positive.
 The negative terminal is identified by a broad strip marked (-) on the body and vice versa.
 The shorter terminal of an unused capacitor is the negative and vice versa.
 The positive terminal is identified by a red spot. (Any 2 x 1)

- (b) (i) **Power rating** = $I \times V$
 = $12 \times 0.8 \text{ A}$
 = 9.6 W (1½ marks)



$$= P = \frac{V^2}{R}$$

$$= R = \frac{V^2}{P}$$

$$= \frac{12^2}{9.6} = 15\Omega$$

(1½ marks)

6. (a) **Transformers**

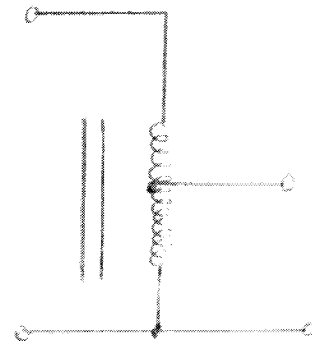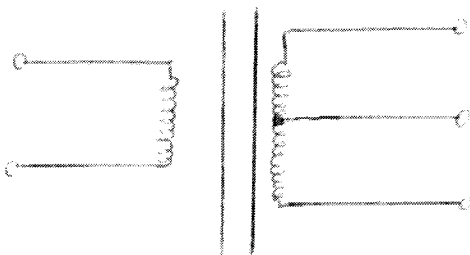

- (b) **Eddy currents** (2 x 1)
 Minimized by - Laminations
 - Insulating material. (2 x 1)

7. (a) **Equipment**
 Meter
 Main fuse
 Sealing chamber
 Armoured cable
 Ripple timer (Any 4 x ½)

- (b) **Protection gear**
 Protects circuit against excess current
 Protects circuit against earth leakage
 Enables isolation of the installation from the supply. (3 x 1)

8. (a) **Uses of LED**
 indicators in instrument panels.
 numerical displays
 lighting
 photocopying (Any 3 x 1)


(b) **Diodes**
 Rectifier diode operates in forward bias.
 Zener diode operates in the reverse bias. (2 x 1)

9. (a) **Indicating instruments** **Method of damping**
 Permanent magnet moving soil - Eddy current
 Moving iron - Air
 Thermocouple - Eddy current
 Electrostatic - Air
 (Any 2 x 1) (2 x 1/2) = 1

(b) **Visual inspections**
 Check for: Broken conductor tracks
 Metal lying across conductor tracks
 Components showing sign of damage - colour
 Dry joints (Any 3 x 1)


10. (a) **Materials**
 + electrode Lead Acid Leclanche
 lead dioxide Carbon
 - electrode lead Zinc
 Electrolyte dilute sulphuric acid Potassium hydroxide (6 x 1/2 = 3)

(b) **Wiring diagram**

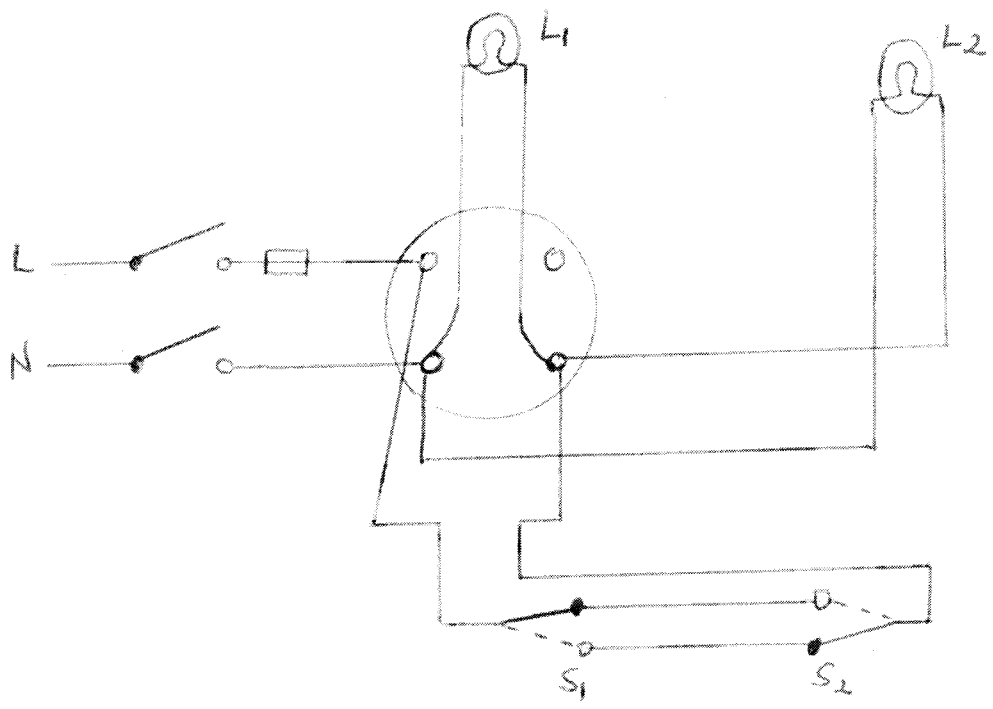

Correct cable routing 1
 Correct circuit 2
 Correct symbols 2

11.

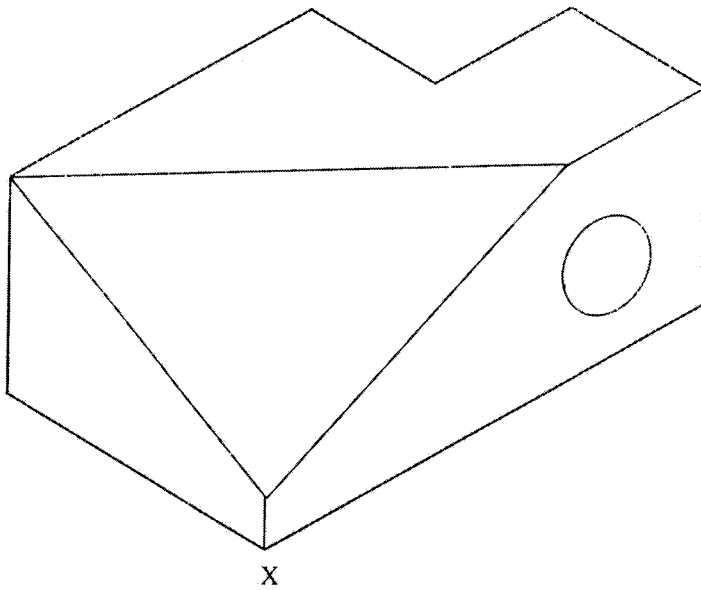

12. (a) $Z = \sqrt{X_L^2 + R^2} = \sqrt{250,000 + 1,000,000}$
 $= 1118 \Omega$

(b) Circuit current $I_T = \frac{V_s}{Z}$
 $= \frac{125}{1118} = 0.1118 \text{ A}$

(c) Voltage drop across:

$$\text{Inductor} = I_T X_L = 0.1118 \times 500 = 55.9 \text{ V}$$

(d) Apparent power = $V_s \times I_T$
 $= 125 \times 0.1118 = 13.975 \text{ VA}$

(e) True power dissipated by resistor

$$P_T = (I_T)^2 R = (0.1118)^2 \times 1000 = 0.0125 \times 1000 = 12.5 \text{ W}$$

(f) Power factor

$$PF = \frac{P_T}{P_A} = \frac{12.5 \text{ W}}{13.975 \text{ VA}} = 0.89$$

(2 x 6 = 12 marks)

13. (a) **Controlling devices**
 Spring control
 Gravity control

(2 x 1)

(b) **Advantages**

- High sensitivity
- Uniform scale
- Well shielded from stray magnetic field


(3 x 1)

(c) (i) Potential drop = $2 \times 200 = 0.4V$
Voltage drop across R = $10 - 0.4 = 9.6 V$
hence $R = \frac{9.6}{0.2} = 48\Omega$

(4 x 1)

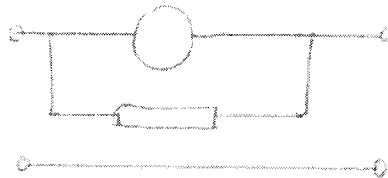
(ii) Low resistance shunt S is connected across the milliammeter shunt carries the rest of the current i.e $10 - 0.2 = 9.8A$

$\therefore 0.2 \times 2 = S \times 9.8 = 0.04 \Omega$




(3 x 1)

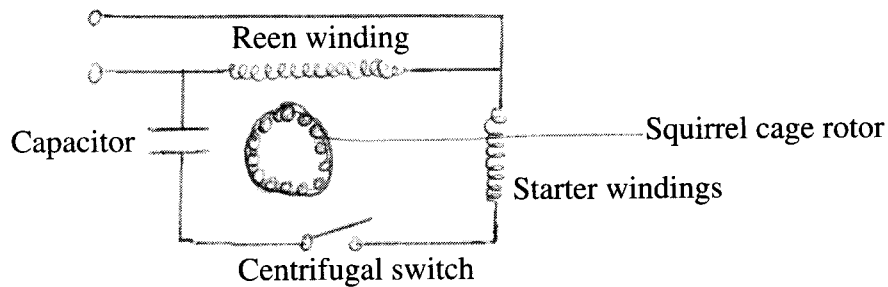14. (a) **Capacitor - start induction motor**



Sketch = 1
Labelling (4 x 1/2) = 2
3 marks

(b)

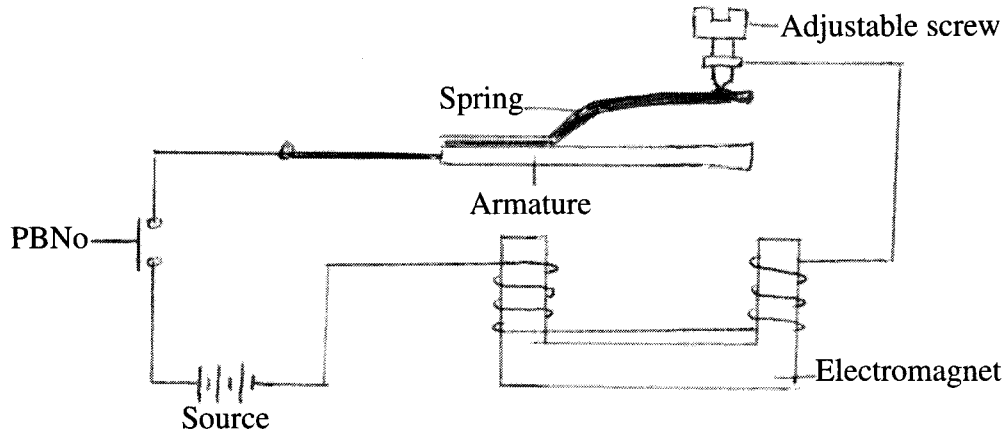

When push button is closed, the circuit is completed. Current flows through the coils which become an electromagnet, and attract the armature. The armature pulls the spring and disconnects the contact points, breaking the circuit and demagnetizing the coils. The armature - spring assembly completes the circuit again and the process is repeated again, creating the buzzing sound at the contacts for as long as the push button remains pressed.

15. (a) (i)

$$\begin{aligned} &= 50 + \frac{(50 + 100) 100}{(50 + 100) + 100} \\ &= 50 + \frac{15000}{250} \\ &= 50 + 60\Omega = 110\Omega \end{aligned}$$

(ii) P.d across R_4

$$\begin{aligned} I_T &= \frac{E}{R_T} \\ &= \frac{22}{110} = 0.2A \end{aligned}$$

1 mark

$I_T = I_2 + I_4$ where I_2 is current through R_2 and I_4 is current through R_3 and R_4 1 mark

$$\begin{aligned} I_4 &= I_T - I_2 \\ \text{P.d across } R_2 &= 22 - I_T R_1 \\ &= 22 - (0.2 \times 50) = 22 - 10 \\ &= 12 \text{ V} \\ \therefore I_2 &= \frac{12\text{V}}{100\Omega} = 0.12\text{A} \\ I_4 &= I_T - I_2 = 0.2 - 0.12 = 0.08 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{P.d across } R_4 &= I_4 R_4 = 0.08 \times 100 \\ &= 8\text{V} \end{aligned}$$