

## 5.6 ELECTRICITY (448)

### 5.6.1 Electricity Paper 1 (448/1)

#### SECTION A

1. (a) **Procedure of connecting an ammeter to take measurements in a circuit**

- Turn - off the power
- Ammeter should be connected in series with the load current.
- Observe polarity.
- Select the range starting from the highest.

$(4 \times \frac{1}{2} = 2 \text{ marks})$

(b) (i) **Nominal resistance**

$$\begin{array}{ccccc} \text{Orange} & \text{Black} & & \text{Brown} & \\ 3 & 0 & \times & 10^1 & = 300 \Omega \end{array}$$

$$\therefore \text{Nominal} = 300 \Omega$$

(1 mark)

(ii) **Maximum resistance**

$$300 + 5\% = 315 \Omega$$

(2 marks)

2. (a) **Circuit diagram**

- Shows connection of every component.
- Shows values of components.
- Shows the position of the components.
- Shows functionality of the circuit.

(any  $2 \times 1 = 2 \text{ marks}$ )

(b) **Bills of materials**

- Materials/parts.
- Quantity.
- Size.
- Estimate costs.

$(4 \times \frac{1}{2} = 2 \text{ marks})$

3. (a) (i) **Forward bias**

reduces  $(\frac{1}{2})$  the PN-junction (depletion layer) and hence the diode conducts  $(\frac{1}{2})$ .

(ii) **Reverse bias**

increases  $(\frac{1}{2})$  the PN-junction (depletion layer) hence the diode does not conduct  $(\frac{1}{2})$ .

(2 marks)

- (b) (i)  $I_{F(max)}$ : is the maximum forward current that the diode can pass without burning out. (1 mark)
- (ii)  $V_{F(typ)}$ : is the forward voltage across the diode at the typical operating current. (1 mark)

4. (a)  $I_p = \frac{V}{R}$   $(\frac{1}{2})$

$$= \frac{100 \text{ V}_{rms}}{1 \text{ k}\Omega} \quad (\frac{1}{2})$$

$$= 0.1 \text{ A} \quad (\frac{1}{2})$$

(b)  $N_1 I_1 = N_2 I_2$  (1)

$$\therefore 1200 \times 0.1 = 400 \times I_2 \quad (\frac{1}{2})$$

$$I_2 = \frac{120}{400} = 0.3 \text{ A} \quad (\frac{1}{2})$$


$$V_2 = I_2 R_2 \quad (\frac{1}{2})$$

$$= 0.3 \times 8000 \quad (\frac{1}{2})$$


$$= 2,400 \quad (\frac{1}{2})$$

(5 marks)

5. (a)

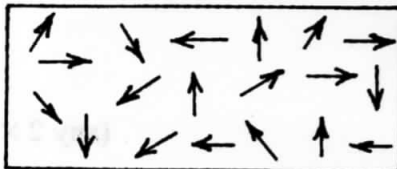

(b)

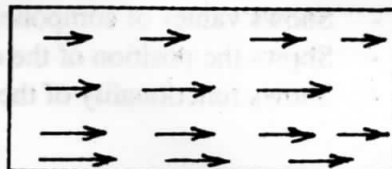

Drawing =  $(\frac{1}{2})$   
 Labelling =  $(\frac{1}{2})$   
 Direction =  $(\frac{1}{2})$   
 =  $1(\frac{1}{2})$  marks

Drawing =  $(\frac{1}{2})$   
 Labelling =  $(\frac{1}{2})$   
 Direction =  $(\frac{1}{2})$   
 =  $1(\frac{1}{2})$  marks

6. (a) (i)  $E = 5 + (I \times R_1)$   $(\frac{1}{2})$

$$= 5 + (2 \times 10^{-3} \times 2000) \quad (\frac{1}{2})$$

$$= 5 + 4$$

$$= 9 \text{ V} \quad (\frac{1}{2})$$

$$(ii) \quad R_2 = \frac{V_2}{I} \quad \left(\frac{1}{2}\right) = \frac{4V}{2mA} \quad \left(\frac{1}{2}\right) = 2 \text{ k}\Omega \quad \left(\frac{1}{2}\right)$$

$$(iii) \quad R_3 = \frac{V_3}{I} = \frac{1V}{2mA} = 0.5 \text{ k} \quad (1)$$

(4 marks)

(b) (i) **Energy consumed**

$$\text{Lights } 5 \times 60 \times 4 = 1.2 \text{ kwh} \quad \left(\frac{1}{2}\right)$$

$$\text{Kettle } 1 \times 2 \times 0.5 = 1.0 \text{ kwh} \quad \left(\frac{1}{2}\right)$$

$$\text{Total energy} = 2.2 \text{ kwh} \quad (1)$$

(ii) **Cost of energy**

$$= 2.2 \times 80 = 1.76 \text{ sh} \quad (1)$$

(3 marks)

7. (a) **Safety precautions to be observed**

- Ensure that the equipment is properly earthed.
- Do not use it in damp areas.
- Always remove the plug from the socket when the equipment is not in use.
- When using extensions, ensure the joints are firm and insulated using the electricians insulation tape.
- Hold it firmly.
- Avoid loose clothing like ties.

(any  $3 \times 1 = 3$  marks)

(b) **Communication service providers in Kenya**

- Telkom Kenya
- Safaricom
- Airtel
- Yu

$(4 \times \frac{1}{2} = 2 \text{ marks})$   
or any other existing ones

8. (a) **Insulating materials used in electrical circuits**

- PVC
- Porcelain
- Magnesium oxide
- Paper
- Rubber
- Air
- Formica

$(4 \times \frac{1}{2} = 2 \text{ marks})$

(b) **Advantages of PVC**

- Easy of erection.
- It is cheap.
- It is resistant to corrosion.
- It is light.
- There is no risk to earth leaks.

(any 3 × 1 = 3 marks)

9. (a) **Inductance required**

$$L = \frac{1}{4\pi^2 f^2 C} \quad \left(\frac{1}{2}\right)$$

$$= \frac{1}{4\pi^2 (1.5 \times 10^5)^2 (10^{-12})} \quad \left(\frac{1}{2}\right)$$

$$= 1.13 \times 10^{-3} \text{ H} \quad 1$$

$$= 1.13 \text{ H}$$

(2 marks)

(b) (i) **Apparent power**

$$= IV \quad \left(\frac{1}{2}\right)$$

$$= 2.5 \times 240 \quad \left(\frac{1}{2}\right)$$

$$= 600 \text{ VA} \quad \left(\frac{1}{2}\right)$$

(ii) **True power**


$$= \text{apparent power} \times \text{power factor} \quad \left(\frac{1}{2}\right)$$

$$= 600 \times 0.6 \quad \left(\frac{1}{2}\right)$$

$$= 360 \text{ w} \quad \left(\frac{1}{2}\right)$$

(3 marks)

10.

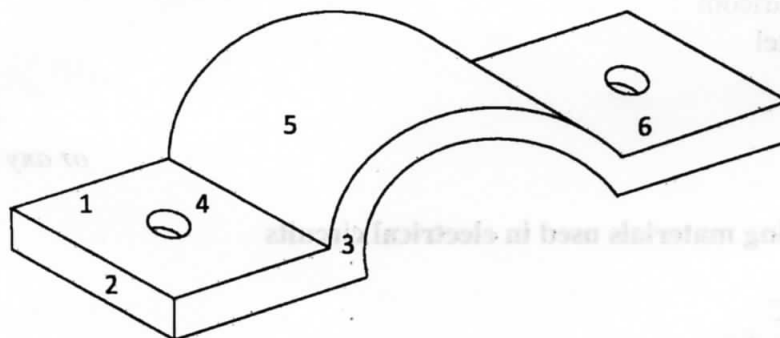


Faces	=	$4 \times \frac{1}{2} = 2$
Holes	=	$2 \times \frac{1}{2} = 1$
Projection	=	1
Neatness	=	$\frac{1}{2}$
Proportionality	=	$\frac{1}{2}$

(5 marks)

## SECTION B

11.

11.

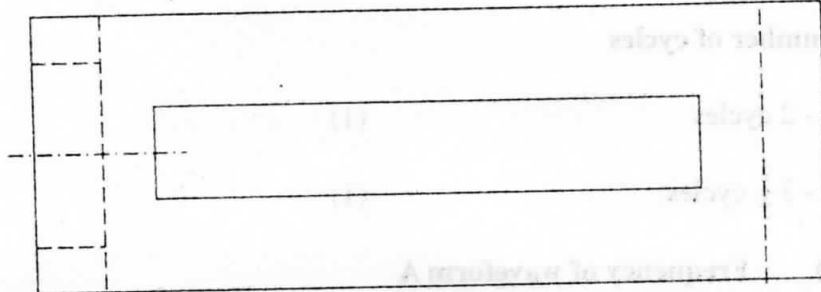


Complete Plan

Faces =  $2 \times \frac{1}{2} = 1$

Hidden details =  $2 \times 1 = 2$

TOTAL 3

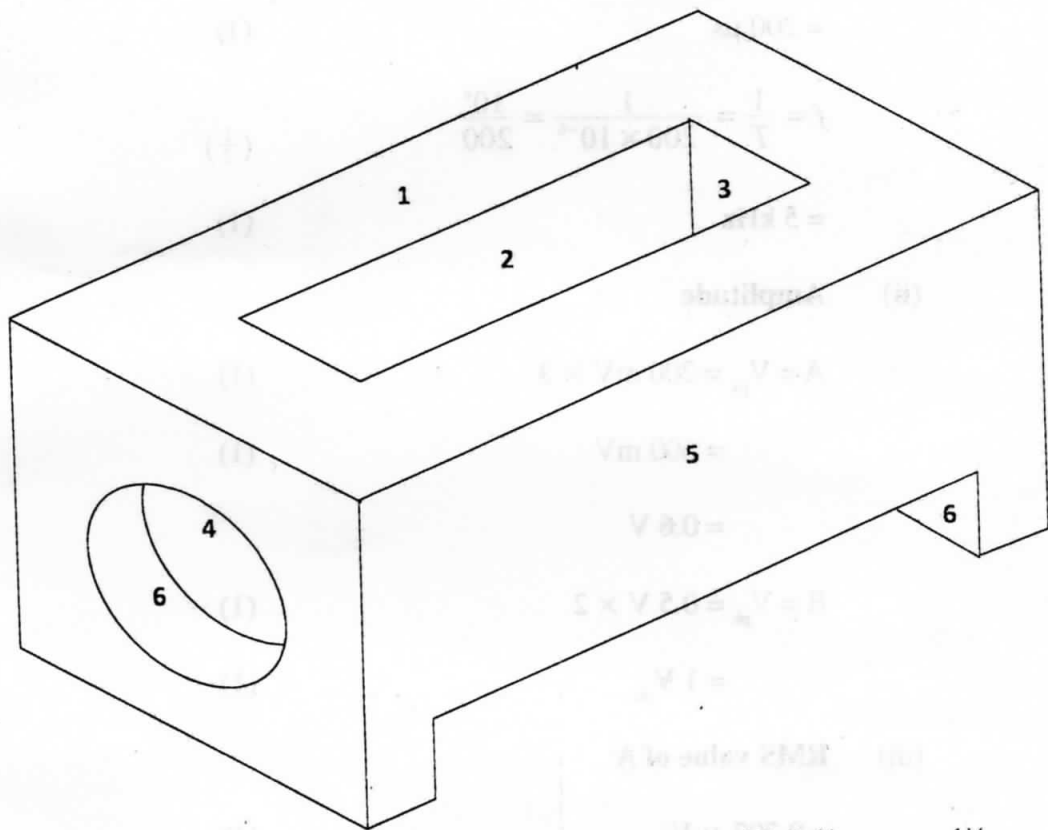

Faces 1, 5 and 7 =  $3 \times \frac{1}{2} = 1\frac{1}{2}$

Faces 2, 3, 4, 6 and 8 =  $5 \times 1 = 5$

Projection = 1

Placement of X =  $\frac{1}{2}$

Neatness =  $\frac{1}{2}$

TOTAL 9



12. (a) **Name of waveforms**

A - sine wave  $(\frac{1}{2})$

B - saw tooth  $(\frac{1}{2})$

(b) **Number of cycles**

A - 2 cycles (1)

B -  $3\frac{1}{4}$  cycles (1)

(c) (i) **Frequency of waveform A**

$$= \frac{1}{T} \text{ where } T = \text{period} \quad (\frac{1}{2})$$

$$T = 50\mu \times 4 \quad (1)$$

$$= 200 \mu s \quad (1)$$

$$f = \frac{1}{T} = \frac{1}{200 \times 10^{-6}} = \frac{10^6}{200} \quad (\frac{1}{2})$$

$$= 5 \text{ kHz} \quad (1)$$

(ii) **Amplitude**

$$A = V_{pk} = 200 \text{ mV} \times 3 \quad (1)$$

$$= 600 \text{ mV} \quad (1)$$

$$= 0.6 \text{ V}$$

$$B = V_{pk} = 0.5 \text{ V} \times 2 \quad (1)$$

$$= 1 \text{ V}_{pk} \quad (1)$$

(iii) **RMS value of A**


$$= 0.707 \times V_{pk} \quad (1)$$

$$= 0.707 \times 0.6$$

$$= 0.424 \text{ V} \quad (1)$$

(13 marks)

13. (a)

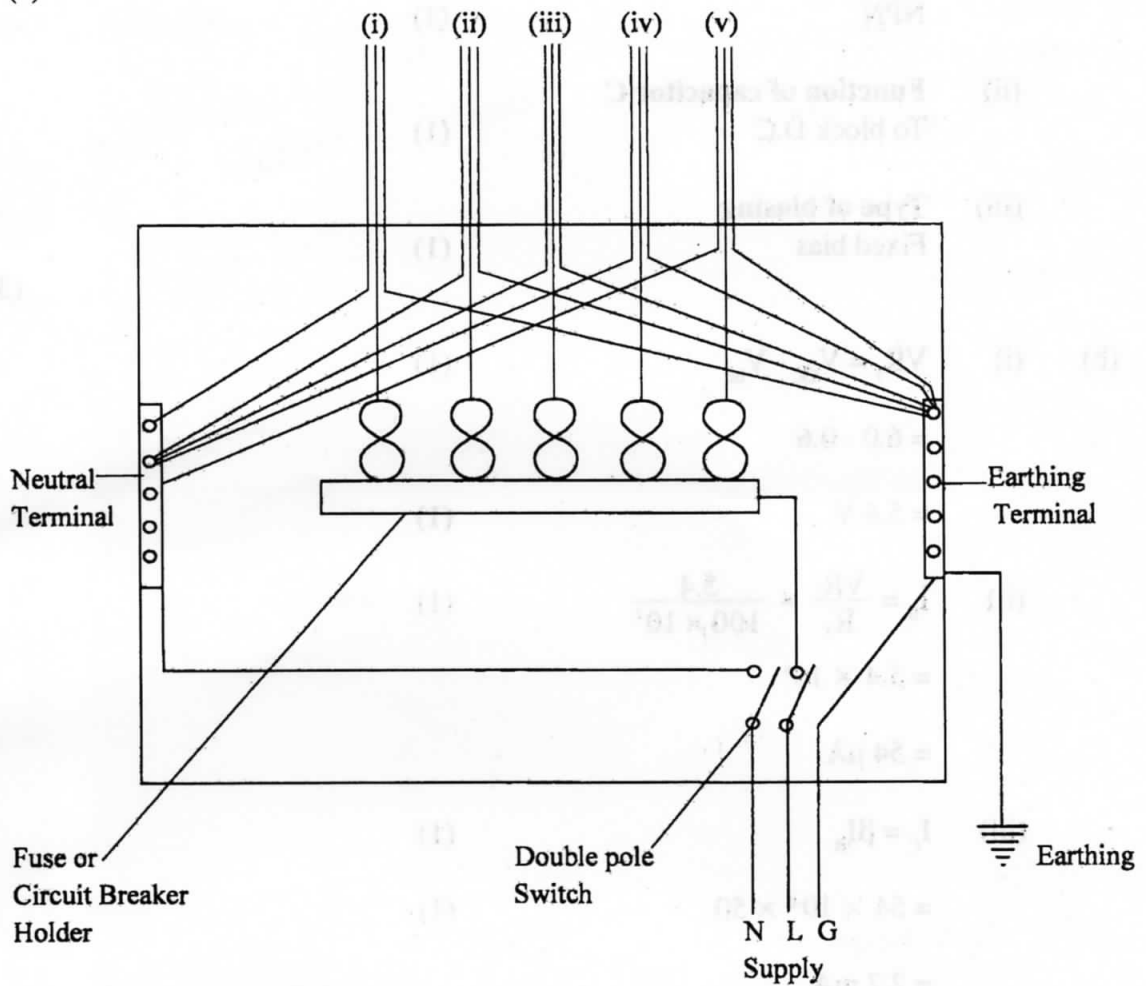

Correct Drawing = 8  
Labelling 6 items = 3

(11 marks)

(b)	(i)	Lighting circuit	=	5 A
	(ii)	Ring circuit	=	30 A
	(iii)	Water heater	=	20 A
	(iv)	Door bells	=	5 A
	(v)	Cooker unit	=	45 A

(any  $4 \times \frac{1}{2} = 2$  marks)

(Total = 11 + 2 = 13 marks)

14. (a) (i) **Type of transistor**  
NPN (1)

(ii) **Function of capacitor C**  
To block D.C (1)

(iii) **Type of biasing**  
Fixed bias (1)

(3 marks)

(b) (i)  $VR_1 = V_{CC} - V_{be}$  (1)  
 $= 6.0 - 0.6$

$= 5.4 \text{ V}$  (1)

(ii)  $I_B = \frac{VR_1}{R_1} = \frac{5.4}{100 \times 10^3}$  (1)  
 $= 5.4 \times 10^{-5}$   
 $= 54 \mu\text{A}$

(iii)  $I_C = \beta I_B$  (1)  
 $= 54 \times 10^{-6} \times 50$  (1)  
 $= 2.7 \text{ mA}$

(iv) **Voltage  $V_{CE}$**   
 $VR_2 = I_C \times R_2$  (1)  
 $= 2.7 \text{ mA} \times 1 \times 10^3$   
 $= 2.7 \text{ V}$  (1)  
 $V_{CE} = V_{CC} - VR_2$  (1)  
 $= 6 - 2.7 \text{ V}$   
 $= 3.3 \text{ V}$  (1)

(10 marks)



15. (a) (i)  $X_L = 2\pi fL$  (1)

$= 2\pi \times 50 \times 0.05$  ( $\frac{1}{2}$ )

$= 15.70 \Omega$  ( $\frac{1}{2}$ )

$X_C = \frac{1}{2\pi fc}$  (1)

$= \frac{1}{2\pi \times 50 \times 2 \times 10^{-6}}$  ( $\frac{1}{2}$ )

$= 1592 \Omega$  ( $\frac{1}{2}$ )

$Z = \sqrt{R^2 + (X_C - X_L)^2}$  (1)

$= \sqrt{1000^2 + (1592 - 15.7)^2}$  (1)

$= 1866 \Omega$  (1)

(7 marks)


(ii) Current =  $\frac{V}{Z}$  (1)

$= \frac{240}{1866}$  (1)

$= 0.12 \text{ A}$  ( $\frac{1}{2}$ ) Amps ( $\frac{1}{2}$ ) (1)

(3 marks)

(b)

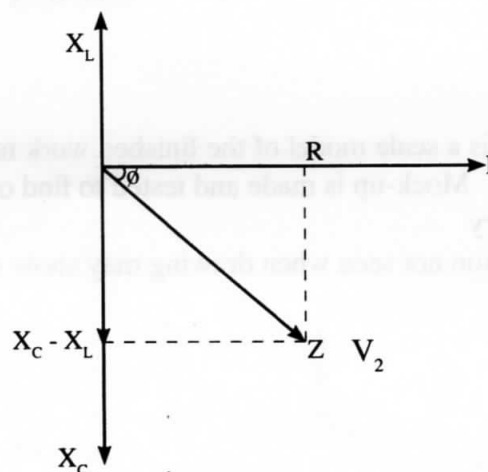

Axes = 1  
Labelling =  $4 \times \frac{1}{2} = 2$

(3 marks)