

4.6 ELECTRICITY (448)

4.6.1 Electricity Paper 1 (448/1)

SECTION A (48 marks)

Answer all the questions in this section in the spaces provided.

1. a) Name **four** equipment belonging to the supply authorities at consumer's intake point. (2 marks)
 (b) List **four** types of capacitors. (2 marks)
2. (a) Draw the circuit diagrams for each of the following d.c. generators:
 (i) Separately excited generator
 (ii) Compound wound generator (4 marks)
3. (a) Name **two** types of semi-conductor diodes and state one application in each case. (2 marks)
 (b) Draw an NPN transistor in common base configuration. (3 marks)
4. (a) Name **three** types of measuring instruments and for each type state their use. (3 marks)
 (b) Sketch each of the following hand tools: (4 marks)
 (i) flat screw driver
 (ii) ball peen hammer
5. Make a free hand oblique drawing of a conduit switch box. (3 marks)
6. (a) List **four** categories of institutions which offer artisan certificate courses in electrical trade. (2 marks)
 (b) Outline the procedures of using a fire extinguisher. (2 marks)
7. (a) State **three** precautions to be observed to avoid accidents from electrical overhead power lines. (3 marks)
 (b) Explain **two** ways of identifying faults in electronic circuits during trouble shooting. (2 marks)

8. (a) State **four** factors that determine the inductance of a coil. (2 marks)
- (b) Two capacitors have capacitances of $6\mu\text{F}$ and $4\mu\text{F}$ respectively. Determine the total capacitance when they are connected in:
- (i) Parallel
 - (ii) Series
- (4 marks)
9. (a) State **two** factors that determine the strength of an electromagnet. (2 marks)
- (b) (i) Draw the sketches of magnetic field around two parallel conductors carrying current in the opposite directions. (2 marks)
- (ii) State what happens between the two conductors in b(i) above. (1 mark)
10. (a) State **two** types of electricity tariffs. (1 mark)
- (b) The average daily power consumption of a domestic consumer is as follows:
- | | |
|-----------------|--------------------|
| Lighting | 1.0 kw for 5 hours |
| Instant shower | 3.0 kw for 2 hours |
| Cooking | 6.0 kw for 3 hours |
| Electric heater | 4.0 kw for 2 hours |
- Determine the:
- (i) daily consumption in kWh
 - (ii) cost of energy in Ksh if the rate is 70 ct per unit (4 marks)

SECTION B (52 marks)

*Answer any **four** questions from this section in the spaces provided.*

11. (a) Define each of the following terms as used in alternating currents:
- (i) Cycle
 - (ii) Frequency
- (2 marks)
- (b) A sinusoidal voltage trace displayed on an oscilloscope has peak to peak voltage of 12 V and a period of 20 ms.
- Sketch and label the waveform. (3 marks)

- (c) A coil of inductance 9.55 mH and resistance 4Ω is connected across a 200 V 50 Hz supply.

Calculate the :

- (i) Inductive reactance
- (ii) Impedance
- (iii) Supply current
- (iv) Phase angle

(8 marks)

12. (a) List **two** accessories used in PVC conduit installation and in each case state their function. (2 marks)
- (b) State **two** possible causes for a fluorescent lamp **not** to start. (2 marks)
- (c) (i) Outline **four** IEE regulations requirements regarding 13A socket outlets. (4 marks)
- (ii) Draw a wiring diagram of a lighting circuit comprising of two lamps L_1 and L_2 controlled by one way switches S_1 and S_2 separately through a joint box. (5 marks)

13. (a) Describe the construction of the following parts of a D.C. machine:

- (i) Yoke
- (ii) Poles

(4 marks)

- (b) A 100KVA, 11 KV/240 V single phase transformer has 800 turns on the primary side.

Calculate the:

- (i) Primary current
- (ii) Number of secondary turns

(6 marks)

- (c) State **three** IEE regulations regarding bell transformers.

(3 marks)

14. (a) Sketch the symbols for each of the following logic gates:

- (i) NAND
- (ii) NOR
- (iii) OR

(3 marks)

(b) **Figure 1** shows a transistor circuit. Take $\beta = 100$ and neglect V_{BE} .

Find the value of V_{CE}

(6 marks)

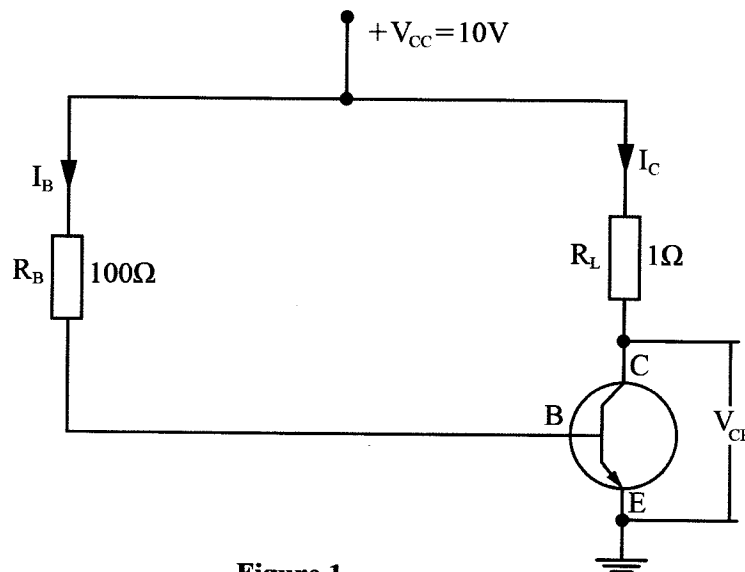


Figure 1

(c) **Figure 2** shows an amplifier circuit whose gain is 100. Neglecting V_{BE} ,

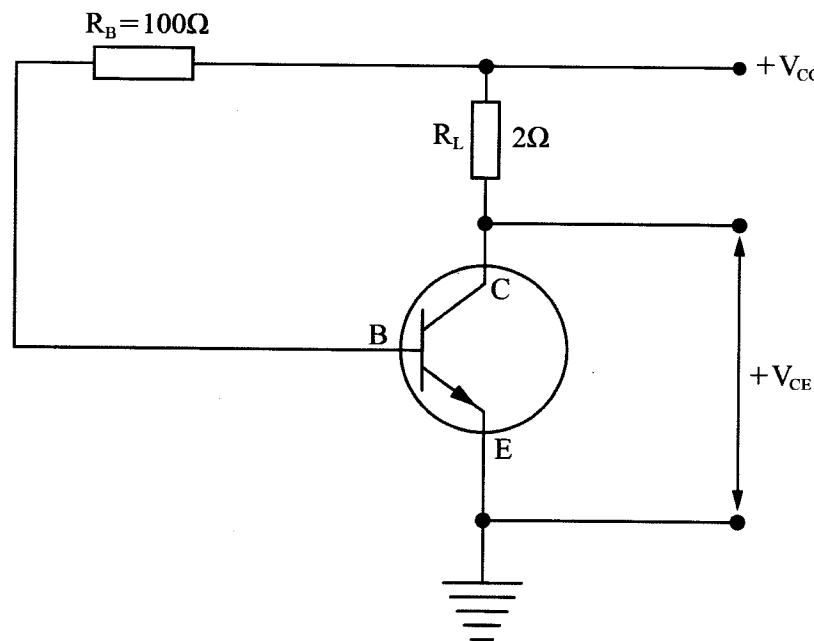


Figure 2

Find the value of:

(i) I_B

(ii) I_C

(iii) V_{CE}

15. **Figure 3** shows three views of a solid drawn in 1st angle projection.
 Draw full size an isometric view of the object making corner X the lowest point. (13 marks)

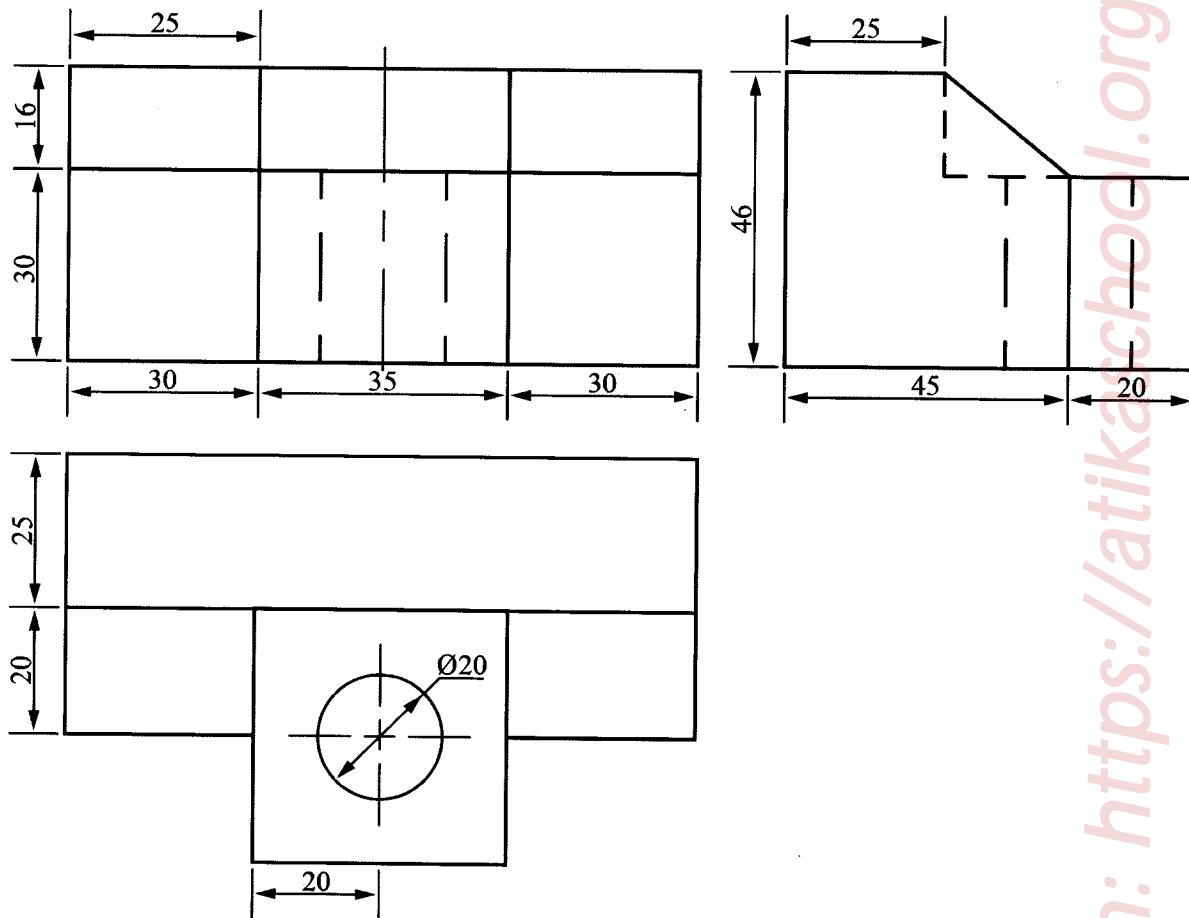


Figure 3

Downloaded From: <https://atikaschool.org>