

5.6.2 Electricity Paper 2 (448/2)

1C	<p>Reasons for differences</p> <ul style="list-style-type: none"> - For parallel circuits - Voltage across the circuit is same - Total supply current $I = I_1 + I_2$ - Total resistance $R_T = \frac{1}{R_1} + \frac{1}{R_2}$ 	<p>1</p> <p>1</p> <p>1</p>
	<p>For series circuit</p> <ul style="list-style-type: none"> - Total supply current is same - Total supply voltage $V = V_1 + V_2$ - Total resistance $R_T = R_1 + R_2$ 	<p>1</p> <p>1</p> <p>1</p>
3C	<p>Tests carried out</p> <ul style="list-style-type: none"> - Insulation resistance test at the plug - Polarity and continuity test for the cable 	<p>1</p> <p>1</p>
4C	<p>Graph</p> <p>Axes – 2 x 1 = 2</p> <p>Plotting – 7 x ½ = 3½</p> <p>Current - 1½</p>	<p>7</p>
d	<p>Determining voltage when LED is ON – 2 x 1 = 2 marks</p>	<p>2</p>