

ALLIANCE HIGH SCHOOL
TERM II ELECTRICITY 448/1
CAT ONE PAPER I
TIME: 2½ hrs

Page of CAT;
Date of returning scripts;
Date of revising scripts;



NAME: CLASS: GRADE: ADMIN:

INSTRUCTIONS:

Answer all questions in section A and any FOUR in section B.
Candidates should have the following for this examination:

- Drawing instruments,
- Calculator / mathematical table,
- Drawing paper size A4.

All dimensions in millimeters.

Do not write on this table

SECTION A	MARKS 48
Discover	Learn
SECTION B	MARKS 52
11	
12	
13	
14	
15	

This paper consists of -17- printed pages.

Candidates should check the question paper to ensure that all the pages are printed as indicated and no questions are missing.

SECTION A (43 MARKS)

Answer all the questions in this section

1.(a) I - List two skills required of an electrical installation wireman. [1marks]

II - State three entry requirements for self-employment in the electrical field.

[1½marks]

(b) Explain the danger posed to each of the following; [2marks]

(i) Engineer works on a rotating machine while his clothes are not buttoned,

(ii) Cable of a soldering iron placed across a pathway,

MANYAM FRANCHISE

Discover! Learn! Apply

(iii) A chuck key is left on the chuck when drilling,

(iv) An engineer's divider is stored in a pocket.

2.(a) Name three protective devices found on a completed electrical installation and explain why they are used. [2marks]

3. (b) Define the following terms. [1½marks]

(i) Saturation in transistors,

When the collector current is increased beyond a certain value, the voltage across the collector-emitter junction remains constant.

(ii) Thermal runaway,

(iii)Extrinsic conduction.

3. (a) Distinguish between the following: [1½marks]

(i) Resistance and reactance,

(ii) RMS value and peak value of AC.

3. (b) State two factors which influence the choice of a motor for a particular application. [1½marks]

Discover! Learn! Apply

4. (a) State **two** applications of each of the following semi-conductors: [3marks]

(i) Transistor,

(ii) Light emitting diode,

(iii)Diode.

(b) State two methods of determining whether a transistor is a PNP or an NPN. [1½marks]

5. (a) Draw the following bias condition of the following transistors:

[3marks]

(i) PNP common base.

(ii) NPN common collector.

(iii) NPN common base.

(b) Explain the half-split method of locating a fault in a multistage amplifier circuit. [2marks]

6. (a) Explain the following terms with respect to a simple Leclanche cell and explain the method to minimize each of the problem; [2marks]

(i) Polarization;

(ii) Local action.

(b) State two junction - bias conditions necessary for a transistor to conduct in a live circuit. [1mark]

(e) Draw and list four equipment at the consumers intake point. [4marks]

7. Calculate the recommended cable size for each of the following final sub-circuits in a domestic installation. [2marks]

(i) Cooker circuit,

(ii) Fuse fitted in a plug of an iron box,

(iii) A light circuit,

(iv) 13A ring power circuit.

(b) What is the purpose of an earth wire in a circuit? [1mark]

MANYAM FRANCHISE

Discover! Learn! Apply

3. (a) Give the reason why a 240V motor whose armature resistance is 0.5Ω draws 15A and not 480A when running at rated speed. [1mark]

(b) Calculate the efficiency of a transformer which delivers 7.5KW of power to a load. The copper losses and iron losses are 150W and 100W respectively. [1mark]

- (c) Figure 1 shows a network of inductors. Calculate; [3marks]
- The total inductance with no mutual inductance.
 - The energy in inductor L_1 and L_2 if currents through them is $2A$ and $4A$ respectively.
 - The total inductance between inductor L_1 and L_3 with mutual inductance of $3mH$ when they are connected in series aiding.

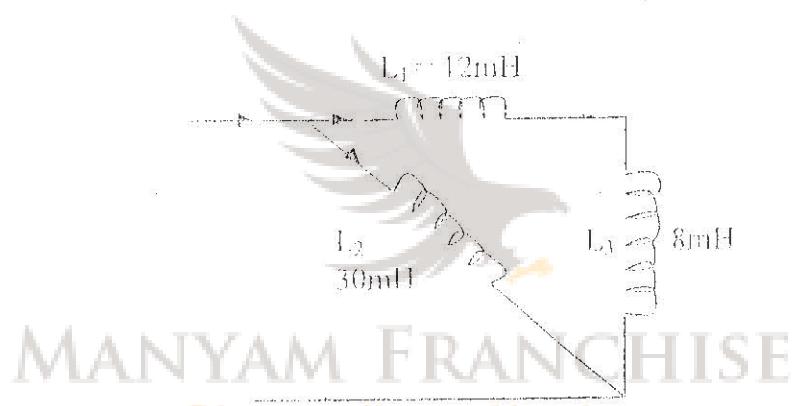


Figure 1.

9. (a) With the aid of circuit diagrams show how three lamps are connected to a common source to achieve each of the following lighting conditions; [2marks]
- Bright light,

- Dim light.

- (b) The range of a moving-iron instrument of resistance 12Ω is extended by using a resistor of 0.0065Ω . If the full scale deflection current is $25mA$, determine the maximum current the modified instrument can measure. [2marks]

- (c) Figure 2 shows a transistor circuit used for switching a $80mA$ bulb. If the gain of the transistor is 120;

(i) Calculate the base current I_B .

(ii) Calculate the emitter current, I_E .

(iii) Determine the load current.

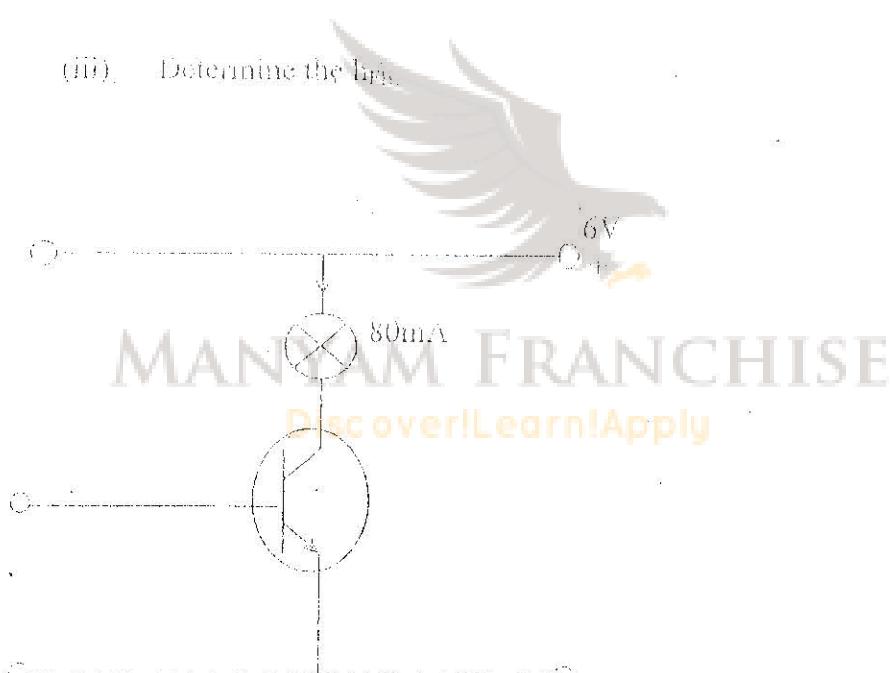


Figure 2

10. (a) Draw a circuit diagram to illustrate how a lamp at the centre of a workshop is controlled from three independent positions. [3marks]

(b) Outline the procedure of carrying out a polarity test on a new domestic installation. [3marks]

(c) Figure 3 shows an RLC circuit. Calculate the total circuit impedance. [3marks]

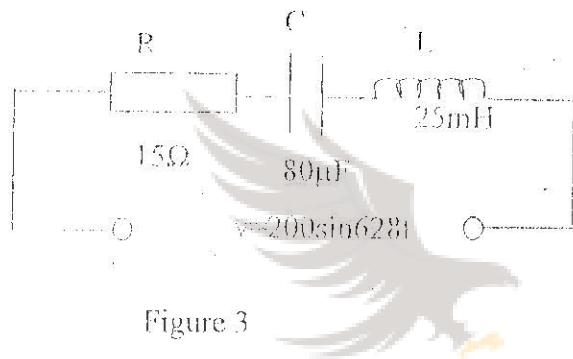


Figure 3

MANYAM FRANCHISE

Discover! Learn! Apply

SECTION B (52 MARKS)

Answer any FOUR questions from this section.

11 (a) For the circuit shown in figure 4, calculate; [4marks]

(i) Collector current,

(ii) Emitter current,

(iii) Emitter voltage,

(iv) Collector - emitter voltage.

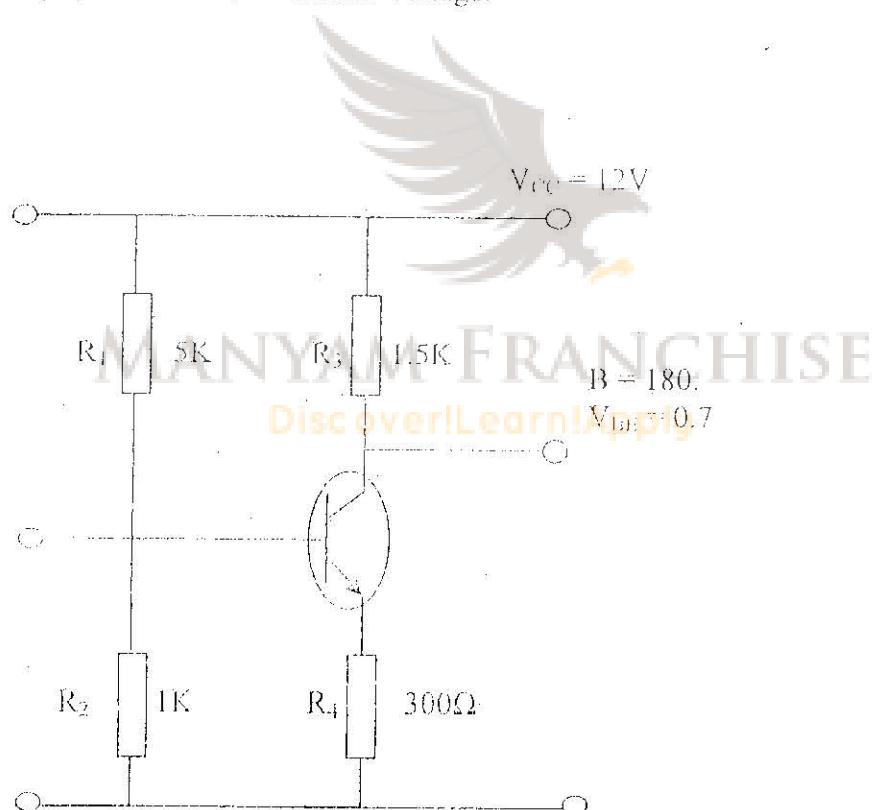


Figure 4

(b) Draw a schematic diagram showing how THREE domestic units are connected to a three phase 4-wire distribution system. Indicate the value of ; [4marks]

(i) A line voltage,

(ii) A phase voltage.

(c) With the aid of a labelled diagram, explain the construction and operation of a capacitor start induction run motor.

{Franchise}



12.(a) Figure 5 shows a drawing of a machine component. On the drawing paper draw in third angle projection the following views; [7marks]

- (i) The front elevation in the direction of arrow Z,
- (ii) Plan,
- (iii) End elevation, include four major dimensions.

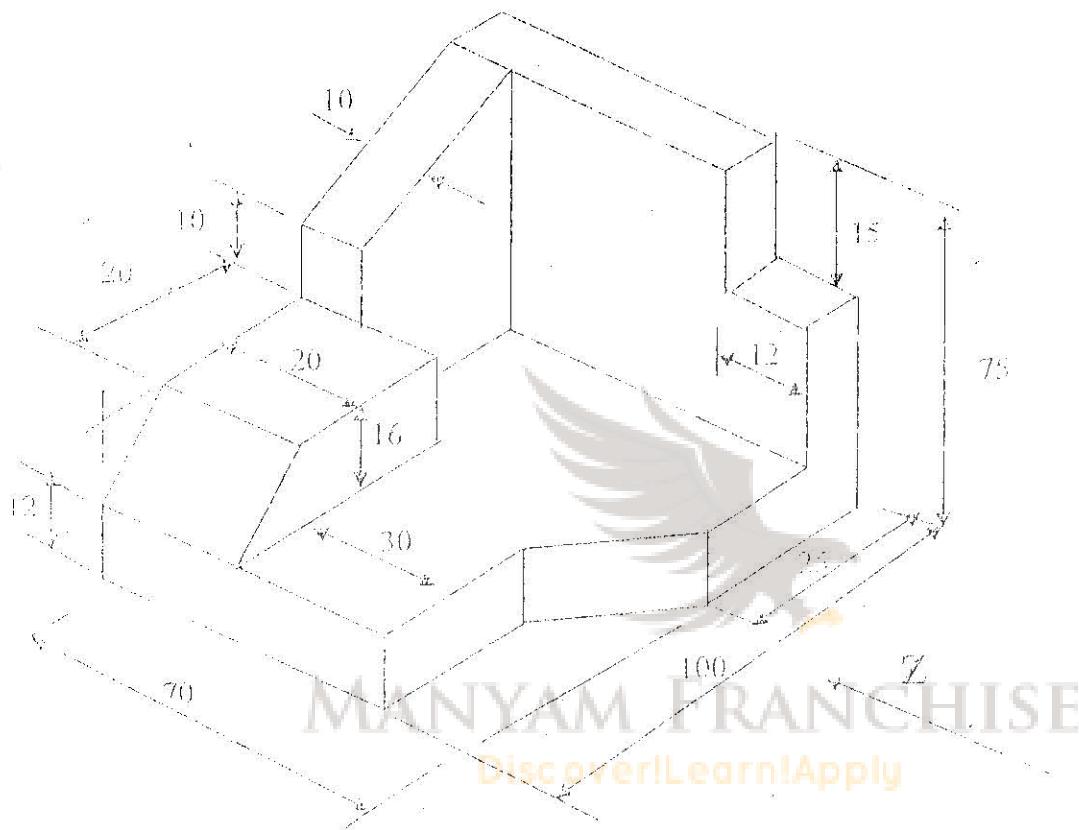


Figure 5

(b) A basic moving coil meter has a resistance of 100Ω and a full scale deflection current of $0.9mA$. calculate; [2marks]

- (i) The value of resistor required to convert it to a $50V$ voltmeter.
- (ii) The sensitivity of the meter.

(c) Sketch and label eight parts of a distribution board.

Remarks

13 (a) A radio receiver circuit is shown in figure 6 below. Name the parts labelled *a* to *f*, and state the function of each. [8marks]

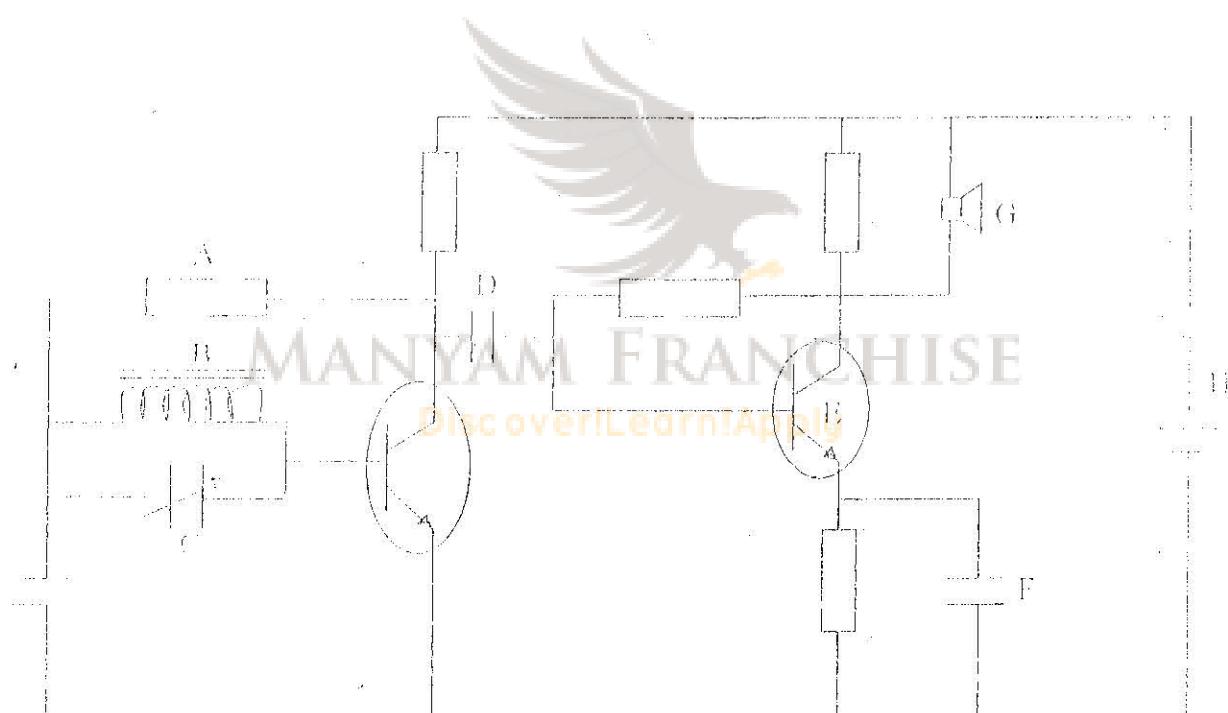


Figure 6

A.....

B The following table summarizes the results of the experiments.

D.....

E.....

F.....

G.....

H.....

(b) Describe four elements of a business plan. [4marks]



MANYAM FRANCHISE

Discover! Learn! Apply

(c) The armature resistance of a shunt motor of 12V dc is 0.5Ω . At rated speed, its brush voltage drop is 1V and armature current is 1.8A. Calculate its back emf. [3mark]

Q4 (a) State ; [2marks]

(i) The maximum power transfer theorem.

(ii) Two areas in which the theorem is applicable.

(b) Figure 7 shows a series parallel circuit. Calculate the: [3marks]
(i) Value of R_3 for maximum power transfer,

(ii) Maximum power transferred to the load,

(iii) Current through the load at maximum power.

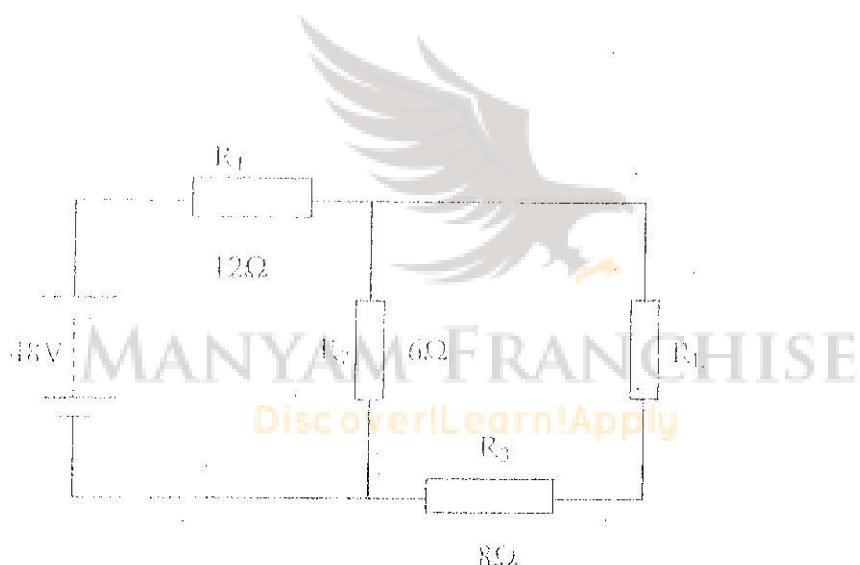


Figure 7

(c) Describe the procedure for installing a lighting final sub-circuit using plastic conduit system on a wooden surface. [4marks]

(d) i- What does the specification 7/0.85 of a cable mean? Calculate the cross section area of the cable [1mark]

If- The graph in figure 8 shows the current – voltage characteristic of a zener diode. [3marks]

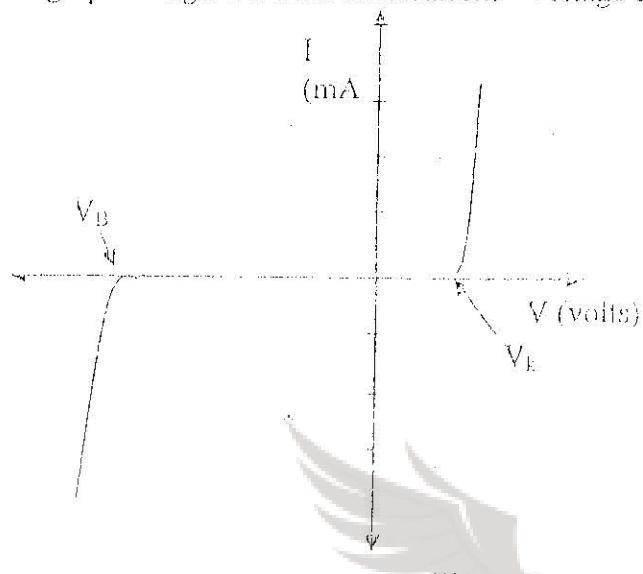


Figure 8

Draw schematic diagrams of the experiment set-up used to determine the curves.

MANYAM FRANCHISE

Discover! Learn! Apply

15 (a) An electrical network is arranged as shown in figure 9 Calculate; [5marks]
(i) The total circuit current,

(ii) Power dissipated in resistors R_4 and R_{45}

(iii) Energy consumed by resistors R_2 and R_5 if the resistor work for 25 minutes

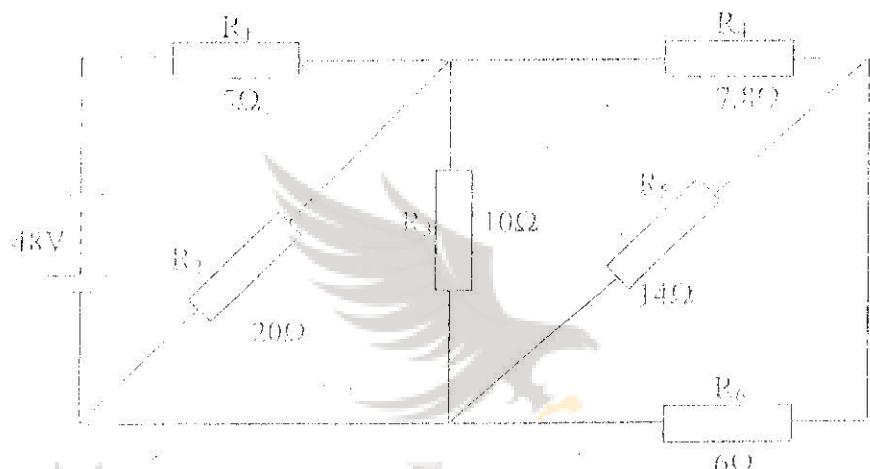


Figure 9

(b) With the aid of a labeled diagram explain the construction and the operation of a step器 in a fluorescent lamp. [diagram]

