

Name: \_\_\_\_\_

Index No: \_\_\_\_\_ / \_\_\_\_\_

1602/204

1522/204

**MICROELECTRONICS, ELECTRICAL  
PRINCIPLES II, INSTRUMENTS AND  
ELECTRONIC FAULT DIAGNOSIS**

Oct./Nov. 2015

Time: 3 hours

Candidate's Signature: \_\_\_\_\_

Date: \_\_\_\_\_



**THE KENYA NATIONAL EXAMINATIONS COUNCIL**  
**CRAFT CERTIFICATE IN ELECTRICAL AND ELECTRONIC TECHNOLOGY**  
**(TELECOMMUNICATION OPTION)**  
**MODULE II**  
**MICROELECTRONICS, ELECTRICAL PRINCIPLES II, INSTRUMENTS**  
**AND ELECTRONIC FAULT DIAGNOSIS**

**3 hours**

**INSTRUCTIONS TO CANDIDATES**

*Write your name and index number in the spaces provided above.*

*Sign and write the date of the examination in the spaces provided above.*

*You should a Scientific calculator/mathematical table and 8080/8085 Instruction set for this examination.*

*This paper consists of EIGHT questions in THREE sections; A, B and C.*

*Answer ONE question from section A, TWO questions from section B and TWO questions from section C in the spaces provided in this question paper.*

*All questions carry equal marks.*

*Maximum marks for each part of a question are as shown.*

*Do NOT remove any pages from this booklet.*

*Candidates should answer the questions in English.*

**For Examiner's Use Only**

Section	Question	Maximum Score	Candidate's Score
A		20	
B		20	
		20	
C		20	
		20	
Total Score		100	

**This paper consists of 24 printed pages.**

**Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.**

## SECTION A: MICRO-ELECTRONICS

Answer **ONE** question from this section.

1. (a) State the function of each of the following microprocessor registers:
- (i) index;
  - (ii) stack pointer;
  - (iii) segment.
- (3 marks)
- (b) List any **two** characteristics of each of the following Intel microprocessors:
- (i) 8085;
  - (ii) 8086;
  - (iii) pentium IV.
- (6 marks)
- (c) A 4 K x 8 RAM memory is implemented using 1 K x 8 memory chips.
- (i) Determine the number of
    - (I) 1K x 8 chips required;
    - (II) Address lines for each 1 K x 8 memory chip.
  - (ii) draw the memory chip organisation.
- (8 marks)
- (d) State **three** advantages of DRAM over SRAM memories.
- (3 marks)
2. (a) Define each of the following microprocessor addressing modes, illustrating each with an example:
- (i) register;
  - (ii) direct;
  - (iii) indexed.
- (6 marks)

- (b) Table 1 shows an assembly language program segment and its corresponding machine code. Fill in the missing data. (10 marks)

Table 1

Address (Hex)	Machine code (Hex)	Instruction	Comment
1800	01 ____	LX1 B, 40 ____	(BC) ← (4030H)
1803	21 50 20	LX1 H, ____	(HL) ← (2050H)
____	____	DAD B	HL ← HL + BC
1807	3E 4E	MV1 A, ____	(A) ← (____)
1809	____ 4A	MV1 B, 4 AH	(B) ← (4 AH)
____	____	ADD B	A ← A + B
180 C	76	HLT	

- (c) Arrange the following microcomputer memories in terms of access times, starting with the fastest: magnetic cassette, DRAM, SRAM, hard disk. (4 marks)

### SECTION B: ELECTRICAL PRINCIPLES II

Answer any TWO questions from this section.

3. (a) (i) State the two methods of damping used in analog instruments.  
(ii) With the aid of a labelled diagram describe spring control of a spindle in moving coil instruments. (9 marks)
- (b) Figure 1, shows a block schematic of a digital voltmeter. Describe its operation. (5 marks)

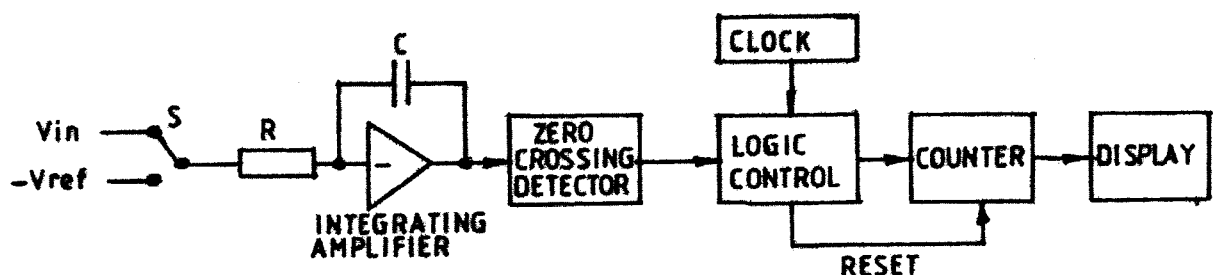


Fig. 1

- (c) A moving-iron instrument requires 400 ampere-turn to give full-scale deflection. Determine the:
- number of turns in the shunt coil to enable the instrument be used as an ammeter reading upto 50 A;
  - number of turns in the multiplier coil to enable the instrument be used as a voltmeter reading up to 300 V;
  - resistance of the multiplier coil.
- (6 marks)
4. (a) (i) Define each of the following with respect to alternating quantities:
- waveform;
  - amplitude.
- (ii) A sinusoidal voltage of frequency 60 Hz has a maximum value of 120 V.
- write down the expression for the instantaneous value of the voltage;
  - determine the time taken by the voltage to rise from 0 V to 96 V.
- (10 marks)
- (b) (i) Draw a circuit diagram illustrating a 3-phase star connected generator feeding a 3-phase star connected load via a 3-phase, 4-wire system.
- (ii) The ratio of the readings of the two wattmeters connected to measure power in a 3-phase balanced load is  $W_2:W_1 = 3:1$ . Determine the load power factor.
- (10 marks)
5. (a) Figure 2 shows a circuit diagram of a parallel R - L network.

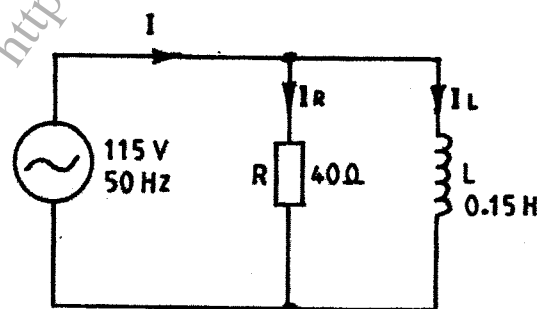


Fig. 2

- (i) Determine the following:
- (I) current through resistor R;
  - (II) current through inductor L;
  - (III) current taken from the supply;
  - (IV) phase angle between the supply current and the supply voltage.
- (ii) Draw the phasor diagram for the circuit using the values determined in 5a(i).  
(12 marks)
- (b) A  $2\ \mu\text{F}$  capacitor is connected to a 100 V dc supply through a  $1\ \text{M}\Omega$  series resistor. Determine the:
- (i) time constant of the circuit;
  - (ii) initial charging current;
  - (iii) voltage across the capacitor after 6 seconds;
  - (iv) time taken for the capacitor to be full charged.
- (8 marks)

### SECTION C: INSTRUMENTS AND ELECTRONIC FAULT DIAGNOSIS

*Answer any TWO questions from this section.*

6. (a) (i) State the function of each of the following controls on an oscilloscope:
- (I) focus;
  - (II) vertical position;
  - (III) volts/division.
- (ii) Explain any **three** measures that should be taken to ensure the safety of test instruments.  
(9 marks)
- (b) With the aid of a labelled diagram describe the calibration of working voltmeter against a standard voltmeter.  
(7 marks)
- (c) A voltmeter having a sensitivity of  $2,000\ \Omega/\text{V}$  is used to measure the voltage across a circuit having an output impedance of  $10\ \text{k}\Omega$ . The open circuit voltage of the circuit is 6 V. Determine the reading on the meter when it is set to a 10 V scale.  
(4 marks)

7. (a) Define each of the following with respect to signal source:

- (i) stability;
- (ii) attenuation;
- (iii) range error.

(6 marks)

(b) With the aid of a labelled block diagram, describe the test for phase distortion in a audio frequency amplifier using a audio frequency signal generator and an oscilloscope.

(7 marks)

(c) A rectangular wave displayed on an oscilloscope has 1 cycle occupying 8 cm on the horizontal scale and its amplitude is 3 cm in the vertical scale. The scale setting on the oscilloscope are 20  $\mu\text{s}/\text{cm}$  and 10 V/cm respectively. For the wave, determine the:

- (i) period;
- (ii) frequency;
- (iii) peak-to-peak value.

(7 marks)

8. (a) (i) State any two faults in electronic circuits that can be revealed by visual inspection.

(ii) Describe the operation of a solder sucker.

(5 marks)

(b) Figure 3 shows a logic circuit diagram of a car seat belt alarm.

(i) State the:

(I) fault that will cause the LED to be ON continuously irrespective of any input state;

(II) symptoms for an open circuit in the pcb track at the output of gate D.

(ii) Explain the effect of an open circuit in the power supply (+5V) line to IC<sub>1</sub>.

(7 marks)

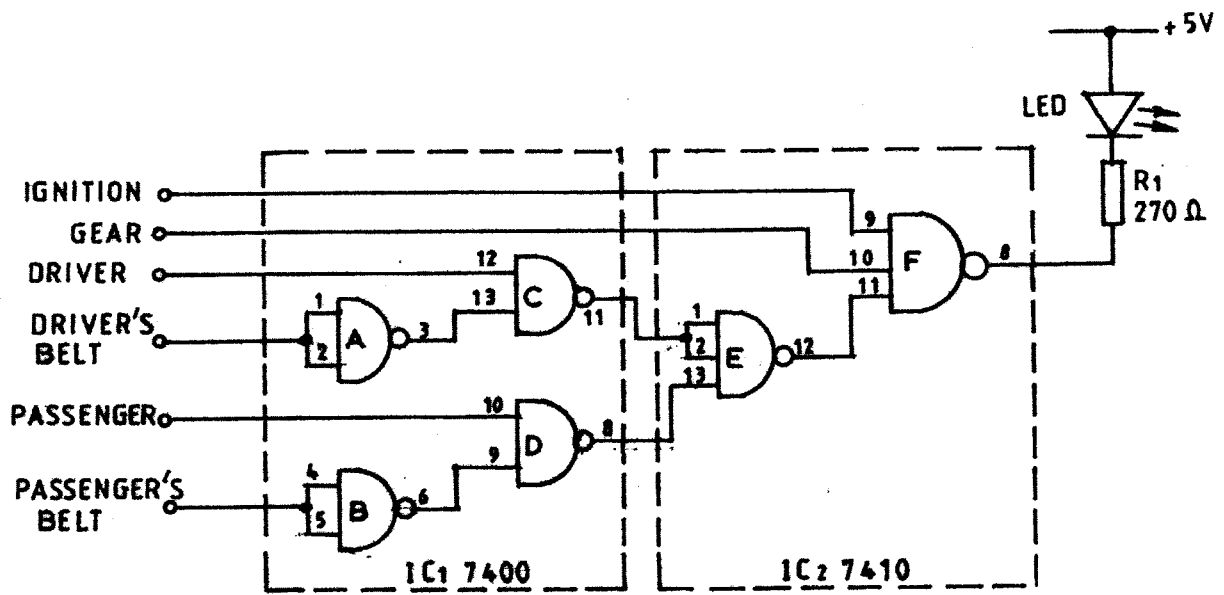


Fig. 3

- (c) Figure 4 shows a circuit diagram of a common base amplifier and table 2 shows the dc bias voltages under normal and fault conditions. State the nature of the fault for each fault condition. (8 marks)


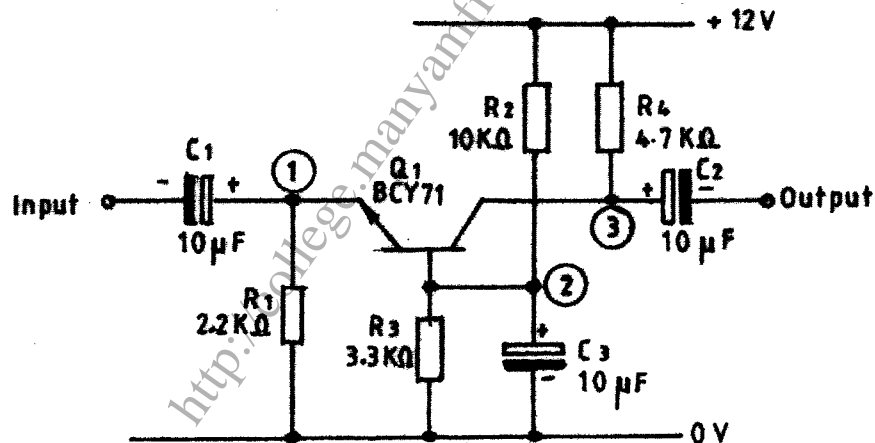


Fig. 4

Table 2

Test point	1	2	3
Normal voltage (V)	2.3	3.0	7.0
Fault A	0	0	12
Fault B	0	3	12
Fault C	3.8	3	3.8
Fault D	5.2	5.9	5.9

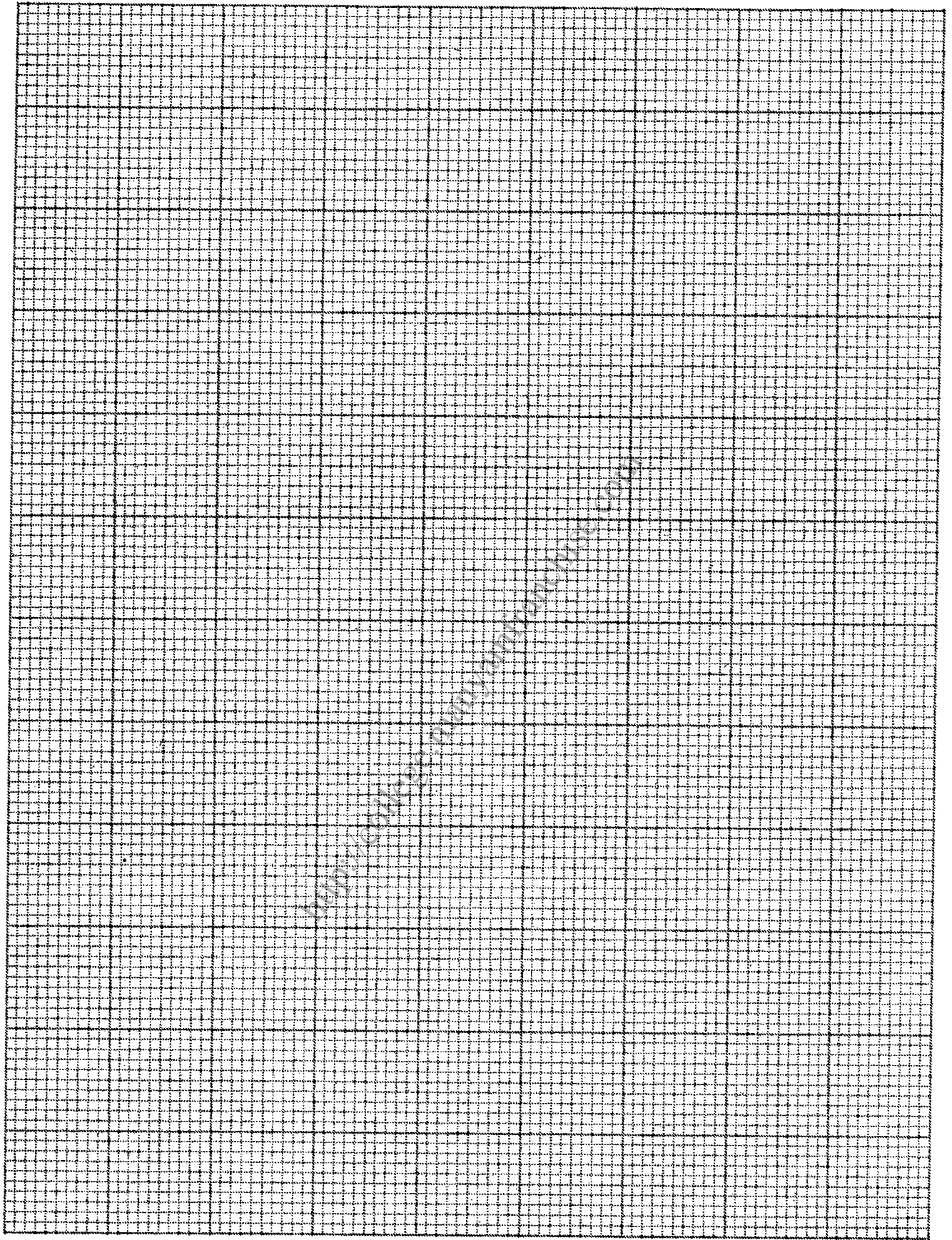



Instruction set of

# 8080/8085

OP CODE	MNEMONIC	OP CODE	MNEMONIC	OP CODE	MNEMONIC	OP CODE	MNEMONIC	OP CODE	MNEMONIC	OP CODE	MNEMONIC
00	NOP	2B	DCX H	56	MOV D,M	81	ADD C	AC	XRA H	D7	RST 2
01	LXI B,D16	2C	INR L	57	MOV D,A	82	ADD D	AD	XRA L	D8	RC
02	STAX B	2D	DCR L	58	MOV E,B	83	ADD E	AE	XRA M	D9	-
03	INX B	2E	MVI L,DB	59	MOV E,C	84	ADD H	AF	XRA A	DA	JC Adr
04	INR B	2F	CMA	5A	MOV E,D	85	ADD L	B0	ORA B	DB	IN DB
05	DCR B	30	SIM	5B	MOV E,E	86	ADD M	B1	ORA C	DC	CC Adr
06	MVI B,DB	31	LXI SPD16	5C	MOV E,H	87	ADD A	B2	ORA D	DD	-
07	RLC	32	STA Adr	5D	MOV E,L	88	ADC B	B3	ORA E	DE	SBI DB
08	-	33	INX SP	5E	MOV E,M	89	ADC C	B4	ORA H	DF	RST 3
09	DAD B	34	INR M	5F	MOV E,A	8A	ADC D	B5	ORA L	E0	RPO
0A	LDAX B	35	DCR M	60	MOV H,B	8B	ADC E	B6	ORA M	E1	POP H
0B	DCX B	36	MVI M,DB	61	MOV H,C	8C	ADC H	B7	ORA A	E2	JPO Adr
0C	INR C	37	STC	62	MOV H,D	8D	ADC L	B8	CMP B	E3	XTHL
0D	DCR C	38	--	63	MOV H,E	8E	ADC M	B9	CMP C	E4	CPO Adr
0E	MVI C,DB	39	DAD SP	64	MOV H,H	8F	ADC A	BA	CMP D	E5	PUSH H
0F	RRC	3A	LDA Adr	65	MOV H,L	8G	SUB B	BB	CMP E	E6	ANI DB
10	--	3B	DCX SP	66	MOV H,M	91	SUB C	BC	CMP H	E7	RST 4
11	LXI D,D16	3C	INR A	67	MOV H,A	92	SUB D	BD	CMP L	E8	RPE
12	STAX D	3D	DCR A	68	MOV L,B	93	SUB E	BE	CMP M	E9	PCHL
13	INX D	3E	MVI A,DB	69	MOV L,C	94	SUB H	BF	CMP A	EA	JPE Adr
14	INR D	3F	CMC	6A	MOV L,D	95	SUB L	C0	RNZ	EB	XCHG
15	DCR D	40	MOV B,B	6B	MOV L,E	96	SUB M	C1	POP B	EC	CPE Adr
16	MVI D,DB	41	MOV B,C	6C	MOV L,H	97	SUB A	C2	JNZ Adr	ED	--
17	RAL	42	MOV B,D	6D	MOV L,L	98	SBB B	C3	JMP Adr	EE	ERI DB
18	--	43	MOV B,E	6E	MOV L,M	99	SBB C	C4	CNZ Adr	EF	RST 5
19	DAD D	44	MOV B,H	6F	MOV L,A	9A	SBB D	C5	PUSH B	F0	RP
1A	LDAX D	45	MOV B,L	70	MOV M,B	9B	SBB E	C6	ADI DB	F1	POP PSW
1B	DCX D	46	MOV B,M	71	MOV M,C	9C	SBB H	C7	RST 0	F2	JP Adr
1C	INR E	47	MOV B,A	72	MOV M,D	9D	SBB L	C8	RZ	F3	DI
1D	DRC E	48	MOV C,B	73	MOV M,E	9E	SBB M	C9	RET Adr	F4	CP Adr
1E	MVI E,DB	49	MOV C,C	74	MOV M,H	9F	SBB A	CA	JZ	F5	PUSH PSW
1F	RAR	4A	MOV C,D	75	MOV M,L	A0	ANA B	CB	--	F6	ORI DB
20	RIM	4B	MOV C,E	76	HLT	A1	ANA C	CC	CZ Adr	F7	RST 6
21	LXI H,D16	4C	MOV C,H	77	MOV M,A	A2	ANA D	CD	CALL Adr	F8	RM
22	SHLD Adr	4D	MOV C,L	78	MOV M,B	A3	ANA E	CE	ACI DB	F9	SPHL
23	INX H	4E	MOV C,M	79	MOV M,C	A4	ANA H	CF	RST 1	FA	JM Adr
24	INR H	4F	MOV C,A	7A	MOV M,D	A5	ANA L	D0	RNC	FB	EI
25	DCR H	50	MOV D,B	7B	MOV M,E	A6	ANA M	D1	POP D	FC	CM Adr
26	MVI H,DB	51	MOV D,C	7C	MOV M,H	A7	ANA A	D2	JNC Adr	FD	--
27	DAA	52	MOV D,D	7D	MOV M,L	A8	XRA B	D3	OUT DB	FE	CP DB
28	--	53	MOV D,E	7E	MOV M,M	A9	XRA C	D4	CNC Adr	FF	RST 7
29	DAD H	54	MOV D,H	7F	MOV M,A	AA	XRA D	D5	PUSH D		
2A	LHLD Adr	55	MOV D,L	80	ADD B	AB	XRA E	D6	SUI DB		

DB = constant, or logical/arithmetic expression that evaluates to an 8-bit data quantity. D16 = constant, or logical/arithmetic expression that evaluates to a 16-bit data quantity. Adr = 16-bit address.