Name___

Index No._____

Candidate's Signature_____

Date _____

1521/204 1601/204 MICRO-ELECTRONICS, ELECTRICAL PRINCIPLES II, ELECTRICAL MAINTENANCE AND FAULT DIAGNOSIS Oct/Nov 2013 Time: 3 hours



THE KENYA NATIONAL EXAMINATIONS COUNCIL

CRAFT CERTIFICATE IN ELECTRICAL AND ELECTRONIC TECHNOLOGY (POWER OPTION) MODULE II

MICRO-ELECTRONICS, ELECTRICAL PRINCIPLES II, ELECTRICAL MAINTENANCE AND FAULT DIAGNOSIS

3 hours

INSTRUCTIONS TO CANDIDATES

Write your name and index number in the spaces provided above. Sign and write the date of the examination in the spaces provided above. You should have the following for this examination:

a non-programmable electronic calculator/mathematical table; 8085 instruction set.

This paper consists of **TWO** Sections: A and B.

Answer ALL the questions in Section A and any ONE question from Section B in the spaces provided in this question paper.

All questions carry equal marks.

Maximum marks for each part of a question are as indicated. Do NOT remove any pages from this booklet. Candidates should answer the questions in English.

Section	Question	Maximum Score	Candidate's Score
A	1	20	
	2	20	
	3	20	
	4	20	
В		20	
1		Total Score	

For Examiner's Use Only

This paper consists of 24 printed pages.

Candidates should check the question paper to ascertain that all the pages are printed as indicated and that no questions are missing.


SECTION A

Answer ALL the question in this Section in the spaces provided.

- 1. (a) Define the following terms as used in D.C. transients:
 - (i) transient time;
 - (ii) time constant.

(b)

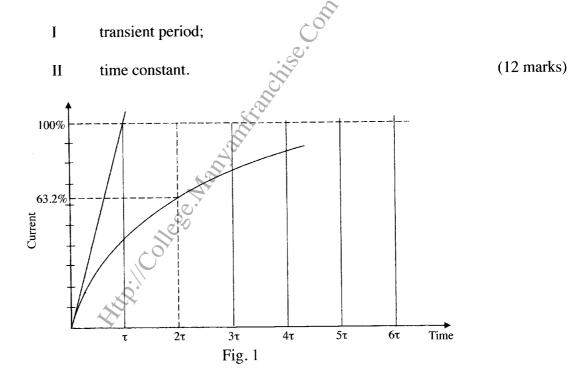- (i) The voltage (V_c) across a capacitor C is initially charged at V volts. It is then discharged through a resistance of R ohms. Show that the voltage V_c is given by the expression: $V_c = Ve^{-t/Rc}$.
 - (ii) Figure 1 shows a typical growth curve of current in an R L circuit where τ = time constant. Determine the:



(c) A d.c. voltage of 120 V is applied across of coil of resistance 8 Ω and inductance 12 H. Determine the value of current, 0.3 seconds after switching on the supply.

(4 marks)

(4 marks)

2.

(a)

(i)

Define the following terms as used in a.c. systems:

- I frequency;
- (ii) form-factor.
- (ii) State any **two** reasons for using sine waves in a.c. circuit analysis. (6 marks)

1521/204 1601/204 (b) Two currents are represented by the expressions:

 $i_1 = 4\sin(\omega t - \pi/4)$ $i_2 = 2\sin(\omega t + \pi/6)$

- (i) draw to scale, on the same axes, the phasor diagram of currents i_1 and i_2 ;
- (ii) using the drawing in (b) (i), determine the sum of currents expressed in the form: $i = I \sin(\omega t \alpha)$. (7 marks)
- (c) A single phase a.c. circuit consists of a coil of inductance 0.05 H and effective resistance 5 Ω connected in parallel with a 0.1 μ F capacitor.
 - (i) Draw the circuit diagram;
 - (ii) Determine the:
 - I frequency of circuit at resonance;
 - II dynamic resistance.
- 3. (a) State the functions of the following microprocessor registers:
 - (i) program counter;
 - (ii) instruction register;
 - (iii) stack pointer.
 - (b) Draw a labelled block diagram of a microprocessor based system and state the function of each block. (9 marks)
 - (c) (i) State the **two** parts on an instruction.
 - (ii) Describe the functions of the following groups of instructions stating **one** example in each case:
 - I data manipulation;
 - II transfer of control;
 - III input/output. (8 marks)

(7 marks)

(3 marks)

4. (a) (i) State:

- I **three** objectives of the health and safety at work act 2007;
- II any **two** steps that a safety engineer or inspector would take when the objectives in (I) above are not observed.
- (ii) Outline **five** precautions taken to safeguard safety of personnel in a workshop environment. (10 marks)
- (b) State any **two** causes of each of the following faults in a d.c. machine:
 - (i) generator fails to excite;
 - (ii) excessive sparking at the commutator;
 - (iii) starter of a d.c. motor fails to hold in ON-position although the motor starts correctly. (6 marks)
- (c) List **four** installation and wiring requirements of electric motors. (4 marks)

SECTION B

Answer any ONE question from this Section in the spaces provided.

(a) (i) Outline the procedure of carrying out routine maintenance checks on a d.c. motor.

- (ii) With the aid of circuit diagrams, describe how the following performance tests are carried out on three phase squirrel cage induction motors:
 - I Nopen-circuit test;
 - II short-circuit test.
- (iii) Describe any **two** abnormal conditions that are likely to occur during the operation of the motors in (a) (ii). (16 marks)
- (b) (i) Explain the reasons for keeping a record of work carried out together with possible test results after a maintenance exercise.
 - (ii) List any **two** test instruments used during maintenance and servicing of equipment. (4 marks)

5.

4

- (a) (i) State the purpose of the following torques in measuring instrument:
 - I damping;
 - II deflecting.
 - (ii) Table 1 shows a comparison of moving coil and moving iron instrument parts. Fill in the missing sections.

Table 1 Type of Instrument	Moving Coil	Moving Iron
Scale	Linear	
Damping		Air
Control	Hairspring	

(iii) State any **three** advantages of digital over analogue instruments. (8 marks)

(b)

A three phase alternator has its windings connected in star. The voltages induced in the windings are:

 $e_{R} = E_{m} \sin \omega t$ $e_{y} = E_{m} \sin(\omega t - 120^{\circ})$ $e_{B} = E_{m} \sin(\omega t - 240^{\circ})$

where Em is the maximum value of voltage:

- (i) draw on the same axis the waveforms to represent the three voltages;
- (ii) show that $e_R + e_y + e_B = 0$. (8 marks)
- (c) Show that the power dissipated in a three phase delta connected load is given by the expression $p = \sqrt{3} V_L I_L \cos \varphi$ watts. (4 marks)
- . (a) Describe the following memory types:
 - (i) primary;
 - (ii) back-up.
 - (b) (i) With the aid of a diagram, explain the operation of a dynamic random access memory cell (DRAM).
 - (ii) State **one** advantage of the cell in (b) (i) over static random access memory (SRAM). (8 marks)

(4 marks)

6.

7.

h

Table 2 shows a 8085 program listing. Using Intel 8085 instruction set, hand code (c) the program, indicating the corresponding memory location.

(8 marks)

Table 2		
ORG	8000 H	
LXI	H 8050 H	
MVI	A 29 H	
MOV	B,A	
MVI	A 23 H	
MOV	C,A	
MVI	A 2 CH	
ADD	С	
MOV	M, A	
SUB	В	
INX	Н	~
MOV	M, A	
HLT	, -	
	I	


8.

State any three common faults in discharge lamp circuits. (a) (3 marks)

- List any two possible causes for each of the following faults in a three phase (b) synchronous motor:
 - (i) smoke emitted from the machine;
 - (ii) shock experienced on touching the casing;
 - (iii) machine does not start when switched on;
 - (iv) machine starts and then stops.

(8 marks)

- In a college workshop, at least two technicians are reported injured every year while (c) carrying out visual inspection on some machines. The maintenance supervisor has come to the realization that this happens because the technicians assume that the machines are stationary.
 - Explain the effect which causes the machines to appear stationary; (i)
 - With the aid of a circuit diagram, illustrate how the effect in (c) (i) may be (ii) minimized. (9 marks)

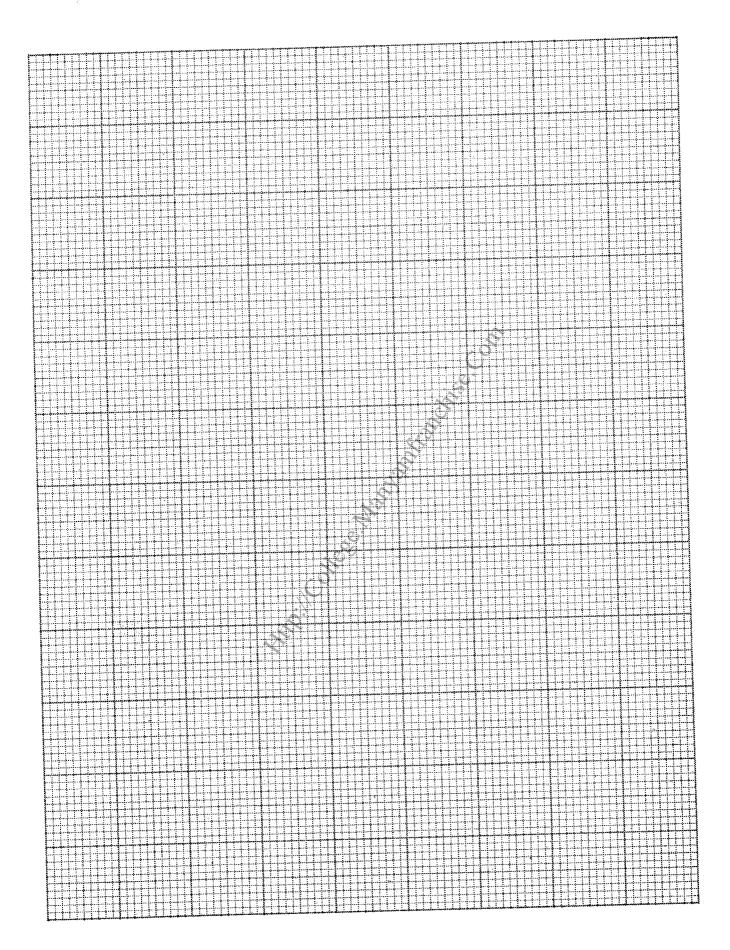

8080/8085

Instruction set of

OP CODE	MNEMONIC		OP CODE	MNEMONIC		OP CODE 56	MNEMONIC MOV D.M		OP CODE	MNEMONIC		OP CODE	MNEMONIC XRA II		OP CODE	MNEMONI	
			28	DCX H					81			AC			D7	NST	2
00 01	NOP LX1	B.D16	20 20	INR	L	50 57	MOV	· .	82	ADD	D	AD	XBA	L	08	RC	
02	STAX	B	20 20	DCR	L	58	MOV	7.	83	ADD	Ε	AE	XRA	М	D9	yan.	
02	INX	B	20 2E	MVI	L,D8	59	MOV	•	84	ADD	н	AF	XBA	A	DA	JC	Adı
03 04	INR	8	2F	CMA	0,00	5A	MOV		85	ADD	1.	B0	ORA	8	DB	IN	08
05	DCR	B	30	SIM		58	MOV	•	86	ADD	М	Bİ	ORA	С	DC	CC	Ad
06	MVI	8.D8	31	LXI	SPD 16	5C	MOV	E,H	87	ADD	A	B2	ORA	D	DD		
07	BLC	5,00	32	STA	Adr	50	MOV		88	ADC	8	B3	ORA	E	DE	SBI	D8
08	~		33	INX	SP	5E	MOV	т. А.	89	ADC	C	84	ÓRÁ	Н	DF	RST	3
09	DAD	8	34	INR	M	5F	MOV		8A.	ADC	D	BS	ORA	L	EO	RPO	
0A	LDAX		- 35	DCR	M	60	MOV		88	ADC	Ç.	B6	ORA	M	E1	POP	H
OB	DCX	8	36	MVI	M.D8	61	MOV		8C	ADC	н	87	ORA	A	- E2	JPO	Ad
.0C	INA	C	37	STC	m,ou	62	MOV		8D *	ADC	L	88	CMP	B	E3	XTHE	
00	DCR	c	38			63	MOV		86	ADC	М	89	CMP	C	E4	CPO	Arl
0E	MVI	C.08	39	DAD	SP	64	MOV		BE	ADC	Α	BA	CMP	D	È5	PUSH	Н
OF	RAC	0,00	3A	LDA	Adr	65	MOV		BG	SUB	в	BB	CMP	£.	E6	ANI	DB
10			38	DCX	SP	66	MOV		91	SUB	C	BC	CMP	H	Ε7	ิศรา	đ
11	LXI	D.D16	1	INR	A	67		HAD	92	SUB	Ø	BD	CMP	L	E8	RPE	
12	STAX	D.	30	DCR	A	68	MOV		93	SUB	E	BE	CMP	М	E9	PCHL	
13	INX	D	3E	MVI	A.08	69	MOV		94	SUB	Н	BF	CMP	А	EA	JPE	Ar
14	INR	D	3F	CMC		6A	MOV	·	95	SUB	L	CO	RNZ		EB	XCHG	ì
15	DCB	D	40	MOV	B,8	66	Mov		96	SUB	М	C1	POP	8	EC	CPE	Ac
16	MVI	D.08	41	MOV	8 C	600	MOV		97	SUB	A	C2	JNŻ	Adr	EO	· · · · · ·	
17	RAL		42	MOV	B,D	60	MOV	-	98	SBB	8	C3	JMP	Adr	EE	ERI	D8
18			43	MOV	8,E \	GE	MOV		99	SBB	С	C'4	CNZ	Adr	EF	RST	5
19	DAD	D	-44	MOV	8,H .	6F	MOV		9A	SBB	D	C5	PUSH	8	FO	RP	
1A	LDAX		45	MOV	BR	70	MOV		98	SBB	E	C6 .	ADI	D8	F1	POP	P\$
18	DCX	D	46	MOV		71	MOV	-	90	SBB	н	°[°_C7	RST	0	F2	JP	A
10	INR	E	47	MOV	B,A	72		M,D	90	588	L	6° C8	RZ		F3	404	
1D	DRC	E	48	MOV		73	MOV		95	SBB	М	C9	RET	Adr	F4	СР	Ą
1E	MVI	E,D8	49	MOV		74	MOV	M.H	9F	SBB	A	CA	۶JZ		F5	PUSH	P
1F	BAR		4A		C,D	75	MOV	M.L	AD	ANA	в	СВ	117 AN 1444		F6	ORI	D
20	RIM		48	MOV		76	HLT	<i>.</i>	A1	ANA	c	cc	cz	Ädr	F7	RST	6
21	LXI	H,D1	1	MOV		77	MOV	M,A	A2	ANA	D	CD	CALL	. Adr	F8	вм	
22	1	Adr	4D	i	C.L	78		A,B	A3	ANA	E	CE	ACI	D8	F9	SPHL	
23	INX	Н	4E		C;M	79		A,C	A4	ANA	1-1	CF	nsr	1	FA	JM	Ą
24	INR	Н	4F	1	C,A	7A		A,D	- A5	ANA	L	DO	RNC		FB	EI	
25	DCR	Н	.50	MOV		78	1	A,E	AG	ANA		D1	POP	Ď	FC	CM	A
26	MVI	H.DØ	1	MOV		70		A,H	A7	ANA		D2	JNC	Adr	FD		
27	DAA		52	MOV		70		A,L	A.8	XRA		D3	OUT	D8	FE	CP1	D
28			53		D,E	7E		A,M	A9	XRA		04	CNC	Adr	FF	RST	7
29	DAD	Н	54		D.H	7F		A,A	AA.	XRA		D5	PUSH	+ D			
÷	1		1	MOV		1	ADD		1		E	D6	SUI	D8	1	ļ	

D8 = constant, or logical/arithmetic expression that evaluates to an 8-bit data quantity. D16 = constant, or logical/arithmetic expression that evaluates to a 16-bit data quantity. Adr = 16-bit address.