

3.20.2 Electricity Paper 2 (448/2)

EXERCISE 1

1. (a) Using materials and equipment provided, connect the circuit as shown in **Figure 1**.

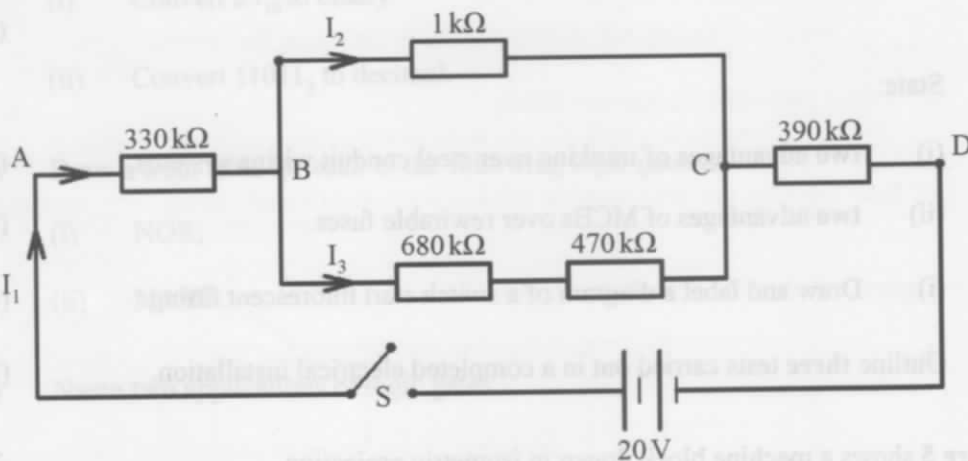


Figure 1

Let the examiner check your work.

(7 marks)

- (b) Close the switch S, measure and record the values of the following quantities in **Table 1**. (6 marks)

Table 1

Quantity		Measured Value	Calculated Value
Current	I_1		
	I_2		
	I_3		
Voltage drop across		Measured Value	Calculated Value
AB			
BC			
CD			

- (c) Calculate and record the corresponding current and voltage values of the measured values. (6 marks)
- (d) Give reasons for the differences between the measured values and the calculated values. (1 mark)

EXERCISE 2

2. Using the tools, materials and equipment provided, fabricate the metallic tray in **Figure 2**. (20 marks)

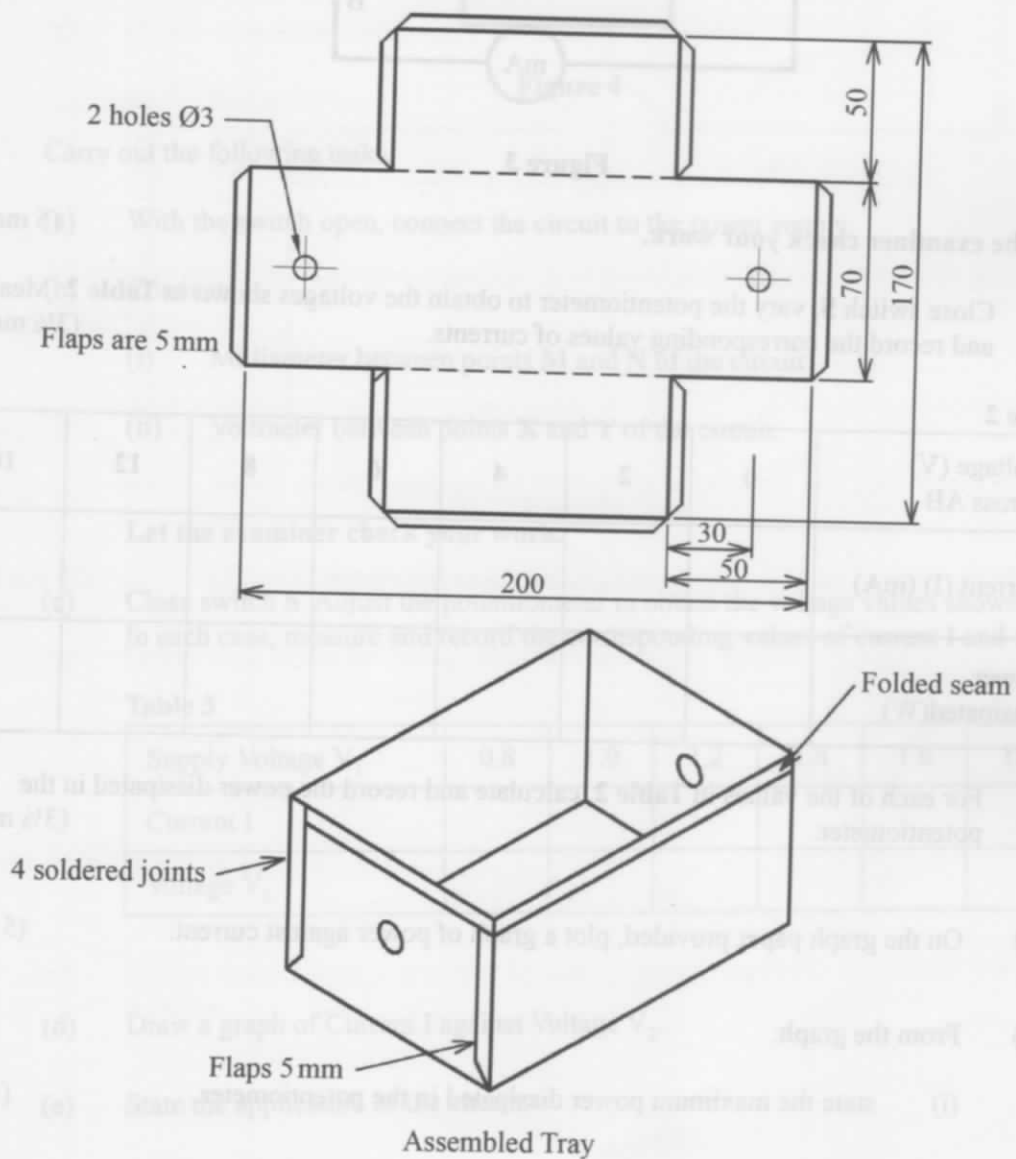


Figure 2

EXERCISE 3

3. (a) Using the materials and equipment provided, connect the circuit as shown in **Figure 3**.

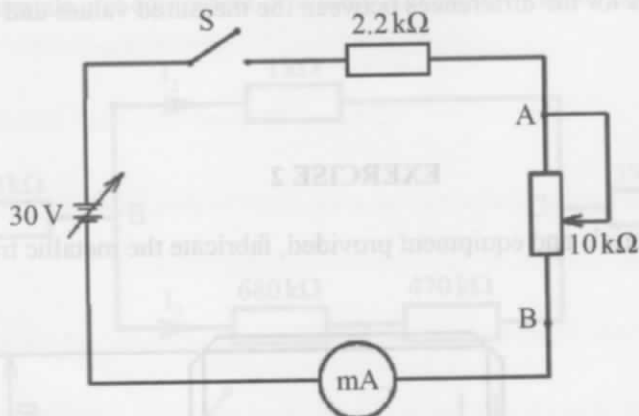


Figure 3

Let the examiner check your work. (5 marks)

- (b) Close switch **S**, vary the potentiometer to obtain the voltages shown in **Table 2**. Measure and record the corresponding values of currents. (3½ marks)

Table 2

Voltage (V) across AB	0	2	4	6	8	12	16
Current (I) (mA)							
Power dissipated (W)							

- (c) For each of the values in **Table 2**, calculate and record the power dissipated in the potentiometer. (3½ marks)
- (d) On the graph paper provided, plot a graph of power against current. (5 marks)
- (e) From the graph:
- (i) state the maximum power dissipated in the potentiometer. (1 mark)
 - (ii) determine the resistance of the potentiometer at maximum power. (1 mark)
- (f) state **one** application of the circuit. (1 mark)

EXERCISE 4

4. **Figure 4** shows the block diagram of a prefabricated circuit **P**.

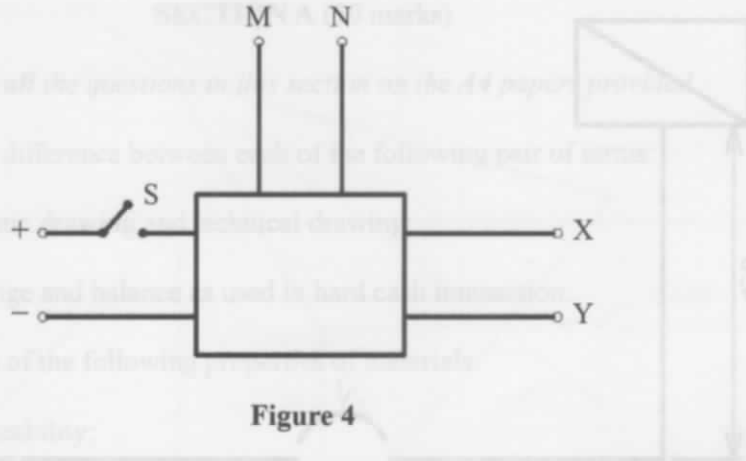


Figure 4

Carry out the following tasks:

- (a) With the switch open, connect the circuit to the power supply.
- (b) Connect:
 - (i) Milliammeter between points **M** and **N** of the circuit;
 - (ii) Voltmeter between points **X** and **Y** of the circuit. (3 marks)

Let the examiner check your work.

- (c) Close switch **S**. Adjust the potentiometer to obtain the voltage values shown in **Table 3**. In each case, measure and record the corresponding values of current **I** and voltage V_2 .

Table 3

Supply Voltage V_1	0.8	1.0	1.2	1.4	1.6	1.8	2.0
Current I							
Voltage V_2							

(7 marks)

- (d) Draw a graph of Current **I** against Voltage V_2 . (8 marks)
- (e) State the application of the circuit. (1 mark)
- (f) Name the device **P**. (1 mark)

EXERCISE 5

5. Figure 5 shows the layout of a power final circuit.

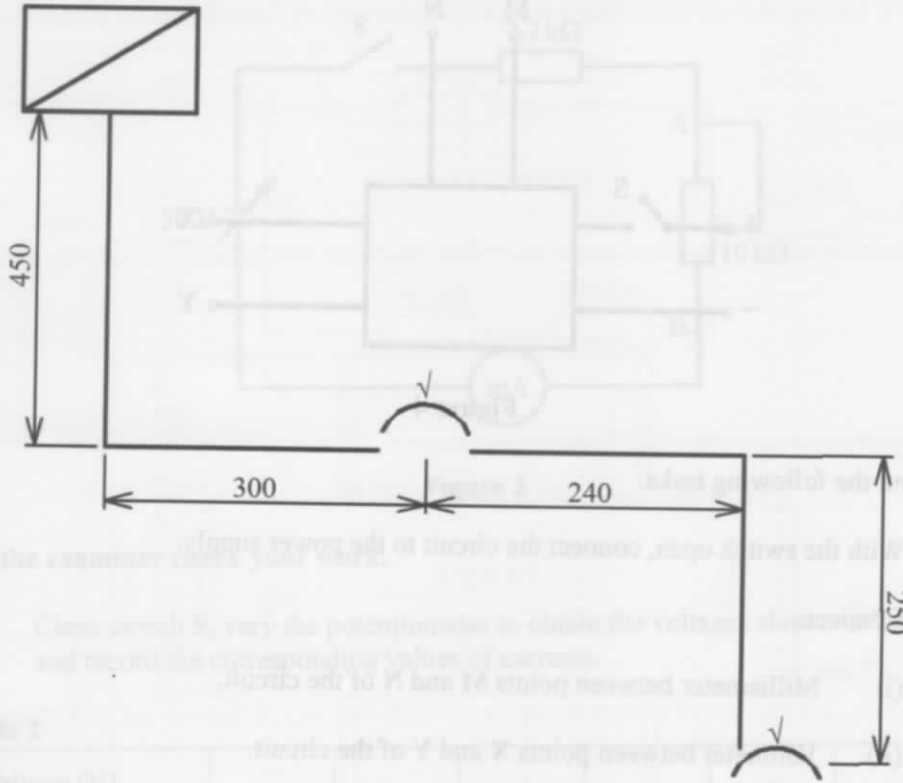


Figure 5

Using PVC sheathed cable wiring system, install the radial circuit. (20 marks)

Supply Voltage V_s	Current I	Voltage V_r
230	1.8	1.8
	1.9	1.9
	2.0	2.0
	2.1	2.1
	2.2	2.2
	2.3	2.3
	2.4	2.4
	2.5	2.5
	2.6	2.6
	2.7	2.7
	2.8	2.8
	2.9	2.9
	3.0	3.0