	wo safety precauti	ons which i	must be ob	servea wne	en using eac	ch of the fol	owing. [4marks]
(i)	Hammer,						
733 4	Coribon				•		
(ii)	Scriber,						
	Control of the Contro						
(iii)	Machines with	exposed ro	tating parts	i.			
	entre (A) and	,	.81	7			
							•
• (iv)	Iron box.		<i>t</i> <sub>s</sub>				
	A Comment of the Comm						
	in the control of the						
· (a) With t	he aid of salemetic	diagrams,	show the i	mproveme	nt needed t	o enable the	,
inistration	(i) ac curre	defic to me: nt.	asure die he	diawing, -			[Towns].
	(ii) ne volta						
•				×			
	The state of the s				•		·
	edicine in		•				
1							
	Secretary and a					,	
	A CONTRACTOR OF THE PERSON OF						•
	-Company						
	# 10 C						
	Salata annua					•	
(b) Define (i)	the following term Doping	S;					[2marks]
* * 7	5.1					•	
•			-				•
(ii)	Intrinsia conduc	tion,					

(iii)   	Pentavalent elements,		
(iv)	Extrinsic conduction.		
(c) List two	applications of each of the following P-N junction diode,	•	[3marks]
(11)	Zener diodes,		•
(iii	Light emitting diodes.		
i. (a) Widi the double	ain of a laveled choun diagram, explain the construction and operation design and operation are also as a second transformer.	er jos <b>i (</b>	of a . [5marks]
The state of the s			
	aible remadies for the following in fluorescent lamps:	•	[3marks]
(b) State twi	possible remedies for the following in fluorescent lamps:  Lamp flickers repeatedly in an attempt to start,		[3marks]
(1)	Lamp electrodes glows continuously but lamp does not light,		-

	(iii	) Lamp does not I	ight at all.					
(c)		the following terms;	•					[2marks]
	(i)	Malleability,						
	(ii)	Ductility,						
	(iii)	Discharge, .						
	(iv)	Lenz's Law.						
5. (a)	With the motor.	e àiu of a fabeled bire	ouit diagram	n inne Sapiete	e e jez iho upora	tion of a s	ni – ni	rosismucz [Smarks]
			•					
	1							
		•						
					N.			
·(c)	List tw	o advantages and two	ı disadvanta	ges of flu	orescent	lamps.		[2marks]

6. (a) Four inductors are connected as shown in figure 1 below. Calculate;

[2marks]

- (i) The equivalent inductance,
- (ii) The energy stored in the inductor  $L_2$  and  $L_4$ ,

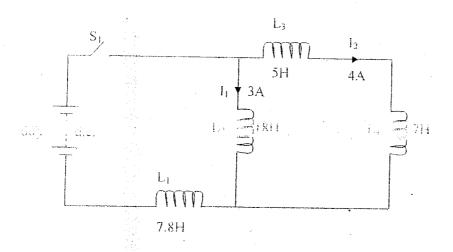


FIGURE 1

(b) List two applications of each of the following devices;

[4marks]

- (i) Electromagnets,
- (ii) Series motor,
- (iii) resistance start induction run motor,
- (iv) Shunt motor.

Calcula	ite the:			,			istance of 400 6mark
(i)	Shunts (	enable the mo	eter measu	re 100mA,	TA and 2F	<b>.</b> .	•
						•	
•							
(ii)	) Multipli	ers to enable	the meter	measure 5	V, 10V and	150V,	, a
		•	ř		•		
· (ii.	i) Draw th	e two multi-	- range me	eters.			
			•				٠
	• •				• • • • • • • • • • • • • • • • • • •	•	
				ngain			
(b) State to	wo functions	of using eacl	n of the follamps,	llowing dev	vices;		[2mark

(iv)

An earth lead.

(c) Explain the following terms used in dis (i) Cold cathode,	charge lamps. [Imarks]
(ii) Hot cathode.	
7. (a) An ac/dc radio was observed to operate Outline four possible causes of the prob	from de batteries but not from live ac mains lem; [2marks]
	en e
(b) Sketch a complete circuit diagram show bias P – N junction.	ing the connection of a forward bias and reverse [2marks]
(c) State the purpose of the following.  (i) An earth electrode.	[2marks]
• (ii) An armouring,	er e
(iii) An earth continuity conductor	

(c) Sta	ate the r (i)	neaning of the following; Fusing factor,	[2marks]
	(ii)	Current rating,	•
	(iii)	Earth lead,	•
	(iv)	Earth electrode.	
9. (a) Dr	aw a lal	beled line diagram of the grid system and indicate all the voltages.	[4marks]
			•
•			
(b) Li	st three	e characteristics of each of the following; Parallel circuits,	[3marks]
	(ii)	Series circuits.	

- (c) List three advantages of each of the following;
  - (i) Dc over ac,

[3marks]

- (ii) Single phase over three phase.
- 10 (a) Figure 2 below show a voltage divider. Calculate;
  - (i) The source emf,

[5marks]

- (ii) Power dissipated by resistors R<sub>4</sub> and R<sub>6</sub>.
- (iii) Energy consumed by resistors R<sub>3</sub> and R<sub>7</sub> after working for 45minutes.

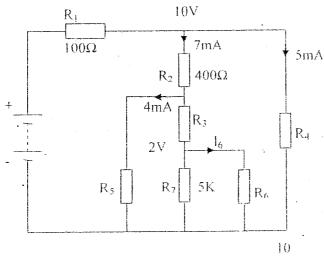


Figure 2

(b) With the aid of a labeled circuit diagram, describe the construction and operation of a magnetic pick - up. [4marks]

(c) Explain how the depletion layer is formed in a P-N junction diode.

[2marks]

11.(a) Two views in figure 3 of a machine plate are drawn in 3<sup>rd</sup> angle orthographic projection.

Draw an oblique pictorial view. Make edge y - y the lowest point. [4marks]

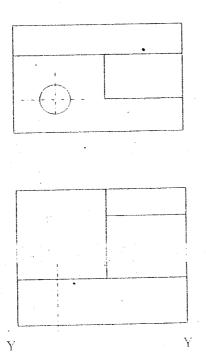


Figure 3